

AMME2700: Instrumentation Lab 1

Resistor Circuit Analysis and High Pass Filters

You need to submit these laboratory notes as a group with all questions answered and all measurements taken down by 2pm, the same day a fortnight after the scheduled day of your lab (Eg. Monday if your session was on Monday). Please submit your finished version to the assignment box near the drawing office of the Mechanical building.

Your Lab's Tutor Name:

Lab Day and Week:

SIDs:

Names:

Introduction

This laboratory is aimed to provide you hands-on experience on building and analyzing basic electronic circuits. You will:

1. Build a resistive circuit and then measure and verify the voltage across each resistor.
2. Build another resistive circuit and then measure and calculate the current through each resistor and the power received by them.
3. Build and analyze a typical first order high pass filter circuit.

All of these exercises will be completed using the ELVIS II experimental kit. ELVIS II is a very powerful general purpose development board containing many useful functionalities. The functionalities that you will use in the ELVIS KIT include:

1. Digital Multi-meter (DMM)
2. Oscilloscope
3. Function Generator
4. Built in 5V power supply
5. Bode Analyzer

Furthermore, there is a breadboard which has exactly the same functionality as any typical breadboard that you can purchase from most electronic shops (Eg. Jaycar). Additional information about the ELVIS II can be found in the user manual: <http://www.ni.com/pdf/manuals/374629c.pdf>

Exercise 1: Voltage Across Resistors (Total 25%)

In this exercise, you will construct a circuit that consists of a number of resistors and then measure the voltage across each resistor.

Procedure

To measure the resistance and voltage, you need to first connect the multi-meter leads to the ELVIS kit at the correct ports. Connect the red multi-meter lead to the $V\Omega$ and the black lead to the COM (ground) port, both ports being located on the left side of the ELVIS kit. After this, open and use the Digital Multi-meter (DMM) software on the computer.

Consider the circuit given in Figure 1. Choose and measure the resistors (Please use resistances $\leq 1.1\text{K}\Omega$ for each resistor to avoid voltage readings from being too small) that you want to use for this circuit. Please note down the resistor values in Table 1 given below. Now build the resistor circuit. Turn on the power supply of the ELVIS II kit and connect the built-in 5 Volt power supply to complete the circuit. Measure the voltage in the direction from the power terminal + to -.

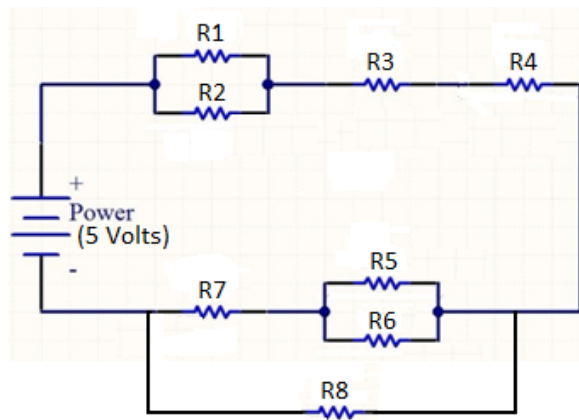


Figure 1: The circuit to be built for exercise 1.

Record your measured values in Table 1. **(10% mark for measurements)**

Table 1: Your resistor values and voltage measurement results.

Resistor ID	Chosen Resistance (Ω)	Measured Voltage (V)	Theoretical Voltage (V) (For Q3, p.3)	Discrepancy (%) (For Q3, p.3)
R1				
R2				
R3				
R4				
R5				
R6				
R7				
R8				

After measuring all your resistor values, please answer the following questions:

1. What was noticed about the voltage in R1 and R2 and also in R5 and R6? What theory explains this observation? Using the same theory, write down all the possible equations for the voltage across R8 in terms of the voltages across R5, R6 and R7. Verify these equations by substituting your voltage measurements into these equations. **(2.5%)**
2. Sum up your voltage around the main loop of the circuit (ie. Calculate $V_2+V_3+V_4+V_5+V_7$). What should this sum equal to and why? **(2.5%)**
3. Please perform (and show) theoretical calculations to recalculate the voltage in all the resistors based on their resistances and report the results in the “Theoretical Voltage (V)” column of Table 1. Please also report the discrepancy between your measured and calculated results as: $e = \frac{V_{Measured}-V_{Calculated}}{V_{Calculated}} \times 100\%$ **(10%)**

Exercise 2: Current and Power in Resistors (Total 35%)

In this exercise, you will build another resistive circuit but this time, the focus is on measuring current and power.

Procedure

To measure current, you need to change the red multi-meter lead to the A port (Just below the COM port). **MORE IMPORTANTLY HOWEVER, when measuring current, you MUST connect the ammeter in SERIES with the resistor of interest! Connecting in parallel will cause a surge in current on the ammeter and may damage the board!!! Remember that ammeters themselves have 0 ohm resistance!**

Consider the circuit shown in Figure 2. Choose and measure the resistors that you want to use for this circuit. Once again, please choose resistance sizes $\leq 1.1\text{K}\Omega$ to avoid obtaining current readings that are too small. Please note that unlike in Exercise 1, you are to use the **15 V power supply** instead for this circuit. Then of course, construct the circuit.

Measure and record the voltage across each resistance as this will be useful later. After this, reconfigure your multi-meter lead connection and measure the current through each resistor. You should measure the current in the direction of from the power terminal + to -. Report all your measurements in Table 2. **(10% mark for measurements)**

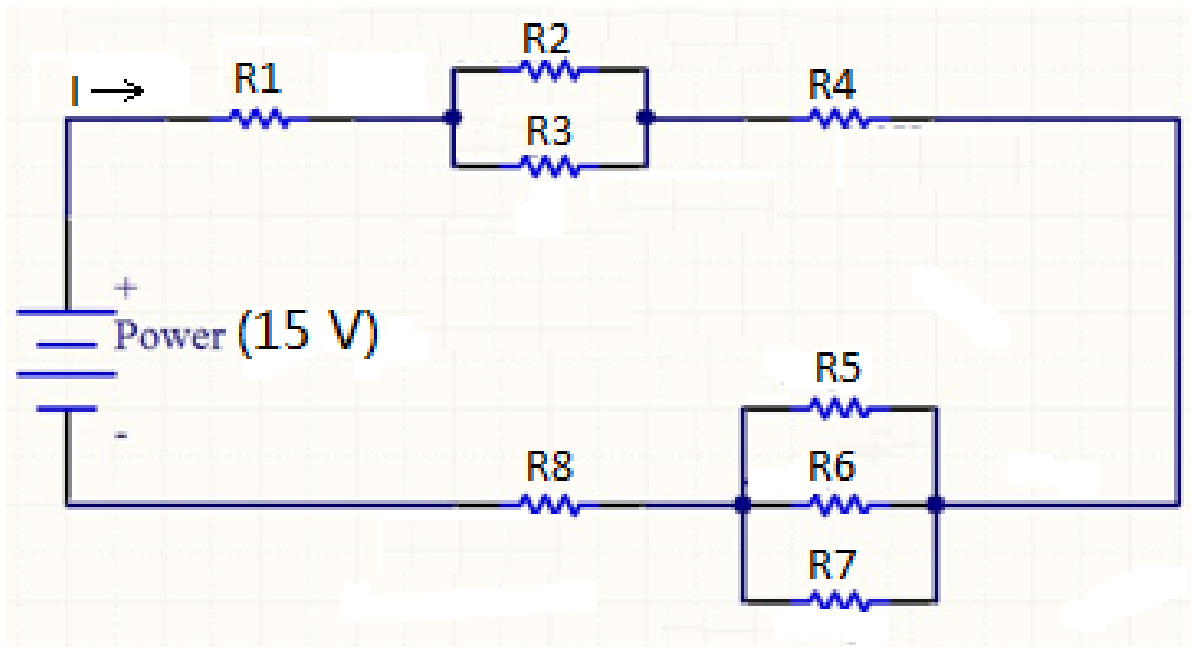


Figure 2: The circuit to be built for exercise 2.

Table 2: Your recorded and calculated results for Exercise 2.

Resistor ID	Chosen Resistance (Ω)	Measured Voltage (V)	Measured Current (A)	Inferred Power (W) (For Q3)	Current by Ohm's Law (A) (For Q4)	Theoretical Current (A) (For Q5)
1						
2						
3						
4						
5						
6						
7						
8						

After performing all the required measurements, please answer the following questions:

1. How much current is being supplied by the power supply? Justify your answer. **(2.5%)**
2. Sum up the currents measured in R2 and R3, then in R5, R6 and R7. What is noticed about the sum of these currents? What theory explains this observation? **(2.5%)**
3. Please state 3 possible equations that can be used to calculate power in each resistor based on your **measured** resistance, voltage and current. Use one of these methods to calculate the power received by each resistor and report the results in the "Inferred Power (W)" column of Table 2. Please also calculate the power that the ELVIS II kit's 5V power supply provided to the circuit based on the current flowing through it. Verify that this supplied power is correct by summing up the calculated powers in each resistor. **(5%)**
4. You may have realized that you can use **Ohm's Law** to calculate the current if you have the measured resistance and voltage of each resistor. Thus, please calculate the current in each resistor based on their measured resistances and voltages and report the results in the "Current by Ohm's Law (A)" column of Table 2. Make a brief comparison of these to your measured current results. **(5%)**
5. Please perform (and show) theoretical calculations to recalculate the expected current in each resistor based on the known resistances and voltage source only and report your results in the "Theoretical Current (A)" column of Table 2. Make a brief comparison of these to your measured current results. (Note that it is not required to report the theoretically calculated voltage and power) **(10%)**

Blank Page for answers to your questions

Exercise 3: High Pass Filters (Total 40%)

Objective

In this exercise, you will learn the concept of an electronic filter. You will study the characteristics of an electronic filter by obtaining the frequency response of a high pass RC filter.

Theory

The impedance of a capacitor is inversely proportional to frequency. This characteristic can be used to select certain frequencies of an input signal. This selection of frequencies is called filtering, and a circuit which does this is called a filter.

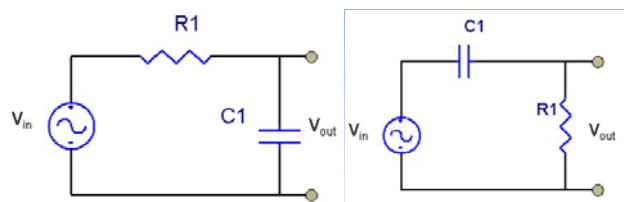


Fig 3: A Low-pass filter

Fig 4: A High pass filter

If a filter passes high frequencies and rejects low frequencies then it is a high-pass filter. Conversely, if it passes low frequencies and rejects high ones then it is a low-pass filter. Filters, like most other systems, are not perfect. They don't absolutely pass some frequencies and absolutely reject others so a clear definition by quantification is required. A frequency is considered passed if its magnitude response (voltage amplitude) is $\geq 70\%$ (or $\frac{1}{\sqrt{2}}$) of the peak input amplitude and is otherwise considered rejected. The frequency which achieves an output of exactly $\frac{1}{\sqrt{2}}V_{input}$ is called the corner frequency, roll-off frequency or half-power frequency.

The corner frequency for a RC filter is given as follows:

$$\text{For RC filter: } f_c = \frac{1}{2\pi RC} \text{ Hz}$$

A bode plot (Fig. 6) is a graph of magnitude of the output voltage of the filter as a function of the input signal frequency. It is used to characterize the range of frequencies in which the filter is designed to operate within. The bode diagram also consists of a phase w.r.t frequency plot where phase is a measure of the delay angle of the output response with respect to the input. Phase diagrams, however, are outside the scope of this lab session.

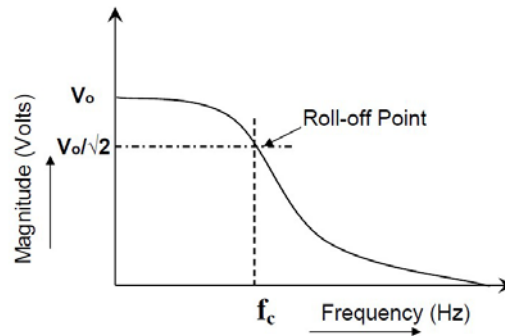


Fig 5: The Bode Plot for a typical low pass filter

In this lab, you will also include an Operational Amplifier (Op Amp) in your filter circuit. Op Amps, as the name suggests, are commonly used for amplifying the input voltage by a constant factor. In your case, however, it is actually used to stop the back flow of electric current so that your filter is protected.

Procedure

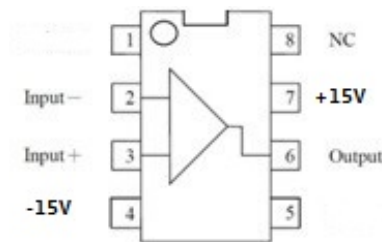


Fig 6: The 741Op Amp pin layout

Construct the first-order high pass filter circuit shown in Figure 7. The pin layout for the Op Amp is shown in Fig 6. Please use C_1 of capacitance 22nF (Use the DMM software to measure capacitance) and R_1 to be between 8000 to 15000 Ohms. R_f shall have the same resistance as R_1 to obtain unity gain. Record the values of these components for future calculations. Use the Function Generator software and apply a 4 V Peak to Peak sinusoidal wave as an input voltage to the circuit.

As seen in Figure 7, AI0 is used to measure the output voltage and AI1 is used to measure the input voltage as a function of time. While the input voltage should be equal to the FGGEN input, it will be measured anyway for verification purposes.

First, you shall use the **bode analyzer program** (accessible from the instrument launcher) to analyze the spectral response of your high pass filter. Set AI0 as the response channel and AI1 as the stimulus channel. Please use a frequency range of 50 Hz to 6 kHz. Then simply hit run.

The resulting bode magnitude curve should begin from a negative dB value and then increases linearly until it reaches the 0 dB point where it levels off. The calculated corner frequency (p. 7) should have a gain of 3 dB less than the level off point. If these results are not obtained, please check your circuit connections and that you switched on the ELVIS II kit's power. **Please take a screenshot and save the magnitude bode plot from the bode analyzer program as you will need this for the questions on page 10. Attach the printed copy of this plot to the end of these lab notes when it is ready for submission.**

You shall now use the **oscilloscope software** directly to measure the spectral response. Begin the experiment with a low frequency (≈ 100 Hz) and measure the input and output peak to peak voltage from the scope screen. Now choose a reasonable frequency increment (Eg. 100 Hz), decide your other input frequencies and make new measurements at those frequencies. Report your results in Table 3. **(20% mark for measurements, including the bode analyzer output)**

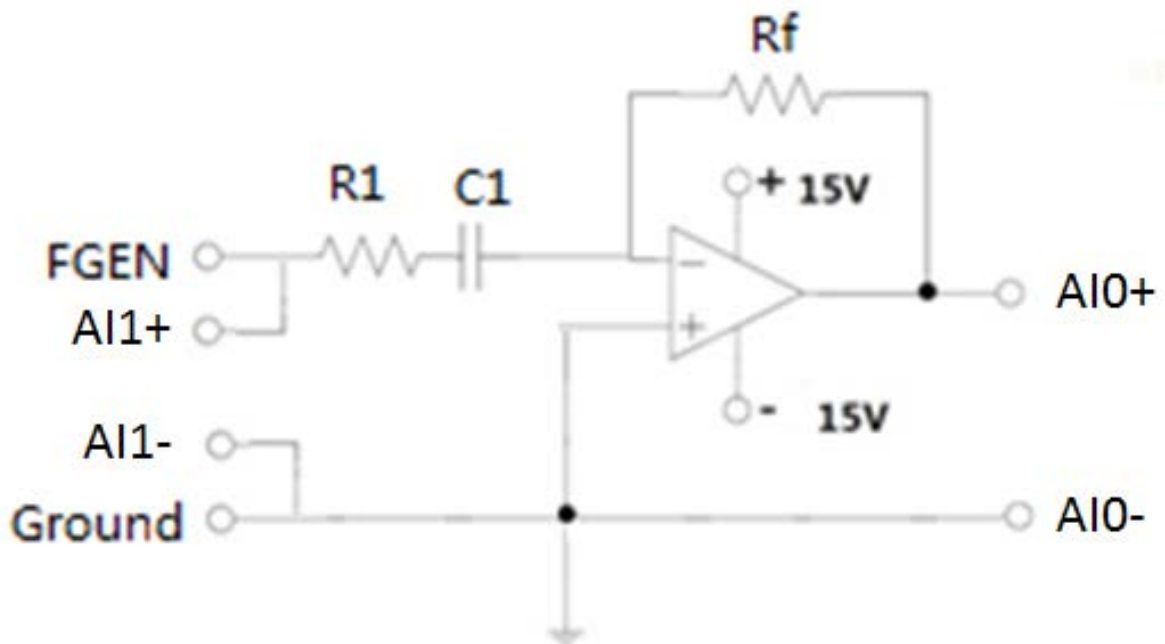


Figure 7: The circuit to be used for Exercise 3

Table 3: Your recorded results for Exercise 3

Measurement No.	Frequency (Hz)	V _{in}	V _{out}	G(V _{out} /V _{in})	20 log(G)
1					
2					
3					
4					
5					
6					
7					
8					
9					
10					
11					
12					
13					
14					
15					

After performing all the required measurements, please answer the following questions:

1. Using your measured results, make a bode plot of the filter using the 20 log (G) values for your y-axis. Compare this with what was found on the bode analyzer program. **(5%)**
2. Estimate f_c based on your drawn bode plot from part (1). Compare this with the theoretically calculated f_c and the one estimated from the bode analyzer program. **(5%)**
3. The transfer function to relate the voltage output to voltage input in this high pass filter is given as:

$$\frac{V_{Out}}{V_{In}} = \frac{R_1 C_1 s}{R_1 C_1 s + 1}$$

Use MATLAB to draw the bode plot for this transfer function (Hint: Type “help bode”, “help bodemag” and “help tf” on MATLAB). Please print this bode plot and attach it to the end of these lab notes. Compare this bode plot to both your experimentally derived one and the one from the bode analyzer program. **(10%)**

Blank Page for answers to your questions

Blank Page for answers to your questions