

# FYS4220

## Real time and embedded data systems

### Introduction to Tools & VHDL



Ketil Røed  
Autumn 2015




# Motivation

- Doing your first FPGA design. (Lab 1).
- Some keywords for this lecture
  - Entity & architecture
  - Signal declaration & assignment
  - Description models (Structural, behavioral)
    - Component and port map
    - non-procedural and procedural (data-flow and process)

# VHDL

*“It is well worth noting that VHDL and other similar hardware design languages are used to create most of the digital integrated circuits found in the various electronic gizmos that overwhelm our modern lives.”*

Mealy and Tepper, “Free range VHDL”

 


# VHDL

- VHDL: VHISC Hardware Description Language
  - VHISC: Very High Speed Integrated Circuits
- Introduced by the US Department of Defence (DoD) in 1981
- Initially a specification and modeling language - documenting behavior of ASICs
  - Alternative to complex manuals
- The idea of simulating this documentation became attractive and logic simulators were developed in the late 1980s.
- The next step was the development of logic synthesis tools to read VHDL and output a definition of the physical implementation of the circuit
- Today it is an industry standard (IEEE 1987) for specifying, verifying and designing digital electronics (library IEEE; use IEEE.std\_logic\_1164.all;)
- Revised VHDL standards: VHDL 93, 2000, 2002, 2007, 2008


 
# VHDL

- VHDL can be looked at as a model of a digital system
  - Powerful alternative to schematic based design
- A change (transition) on the input may lead to a new system state and consequently a change of the output after a given time delay
- Describes and simulates concurrent events



Representation of a digital system

# Important remarks

- VHDL is a **HARDWARE DESCRIPTION LANGUAGE**
- **You are designing actual hardware!**
- A VHDL model is translated into actual hardware and mapped onto a CPLD/FPGA
- Due to the nature of hardware components which are always running, **VHDL is a highly concurrent language.**
  - Simultaneously execution of several tasks
- This is in contrast to other high level languages where the code is executed (sequentially) by a processor (predefined hardware).
- Execution of a VHDL code means that the VHDL model is being simulated (by software running on a computer)



# Design approach



- VHDL descriptions of circuits are based on the black-box approach.
- The two main parts of any hierarchical design are the black box and the stuff that goes into the black box (e.g. other black boxes)
- In VHDL the black box is referred to as **entity** and the stuff that goes inside it is referred to as the **architecture**.
- Allows to use hierarchical structure (modularity) and the reuse of previously written code.
- A module is referred to by its inherently simple black box representation rather than by the details of its inside circuitry
  
# Compared with an IC


- The **entity** describes the interface to the outside world (connection pins of package)
- The **architecture** describes the functionality of the circuit inside the entity (package)



# Entity & architecture templates

```
entity model_name is  
port  
(  
    list of inputs and outputs  
);  
end model_name;
```

Same name as the file,  
e.g. **module\_name.vhd**



---

```
architecture architecture_name of model_name is  
begin  
    ...  
    VHDL concurrent statements  
    ....  
  
end architecture_name ;
```

# Entity declaration


- Abstract the functionality of a circuit description to a higher level.
- Provides a wrapper for the lower-level circuitry

```
entity AND_GATE is  
port (A: in std_logic;  
      B: in std_logic;  
      Y: out std_logic);  
end;
```

Unique  
Identifier  
name


direction

Type of data

 
 
# Direction (mode)


- **In** – flow into the entity
- **Out** – flow out of the entity, **no** feedback
- **Buffer** - flow out of the entity, feedback allowed
- **Inout** - for bi-directional signals


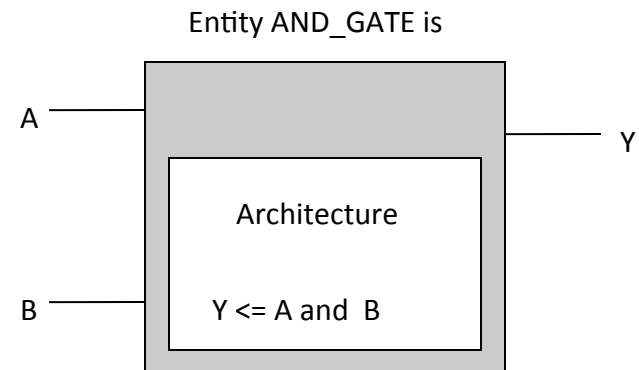
# Architecture



- While **entity** describes the interface or external representation of the circuit, the **architecture** describes what the circuit actually does
  - Defines structure/behavior of the entity
- Entity declarations are generally easy while describing the operation of a circuit can become very complex

```
architecture struct of AND_GATE is
--Deklarasjons område
--Kan bestå av f.eks Typer, signal, komponent
begin
Y <= A and B;
end;
```





# Example of basic AND-gate

  

```
library ieee;  
use ieee.std_logic_1164.ALL;
```

```
entity AND_GATE is  
  port (A: in std_logic;  
        B: in std_logic;  
        Y: out std_logic);  
end;
```

```
architecture struct of AND_GATE is
```

```
begin  
  Y <= A and B;  
end;
```

# Main VHDL object types

- **Signals**
  - communication between components
  - Software representation of a wire (real physical signal)
  - Signal assignments are associated with a delay
- **Variables**
  - Convenient mechanism for local storage
  - E.g. loop counters, intermediate values
  - All assignments take place immediately (no delay)
- **Constants**
  - Is like a variable object but the value cannot change

# Declaration and assignment

- Needs to be declared before they are used
- Declaration of
  - **Signals** are done inside the scope of the architecture (cannot be declared inside a process)
  - **Variables** can only be done inside a process
  - **Constants** can be done in architecture and inside process
- Assignment of a new value to a
  - **Signal** is done using the operator " $\leq$ "
  - **Variable** is done using the operator " $:=$ "
- Variable assignments are executed instantaneously while signal assignments are executed after a certain time

# Identifier

- Identifier is the name of an object (e.g. signal)
- Names can be constructed using:
  - a b c ... z (alphabetic letters)
  - 0 1 2 ... 9 (numbers)
  - \_ (underscore)
- With the following reservations:
  - The first character must be a letter
  - The last character cannot be an under score
  - Successive underscores are not allowed
  - Cannot use VHDL reserved words (e.g. **and**, or, **port**, **constant**)
- VHDL is case insensitive
- nextstate ⇔ NEXTSTATE ⇔ nExTsTaTe

```
entity AND_GATE is
port (A: in std_logic;
      B: in std_logic;
      Y: out std_logic);
end;
```

# Arithmetic & logical operators

## Arithmetic operators

- + Addition
- - Subtraction
- \* Multiplication
- / Division



Use with care, creates much logic

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use ieee.numeric_std.all;
```

## Logical operators:

- and, nand, or, nor, not, xor, xnor
- IEEE 1164 uses these operators in **std\_logic**

# Logical operators

- **and, or, not, nand, nor, xor og xnor** are predefined for **bit, boolean, std\_(u)logic**,
- Logical operators (except **not**) do not have precedence in VHDL, therefore parenthesis is demanded in multi level logic:
  - **X <= A or B and C** gives an error in VHDL (equal precedence of operators)
  - **A or (B and C)**
  - **(A or B) and C**

Correct for VHDL

- **not A and B** This is the same as:
- **(not A) and B** **not** has higher precedence than **and**, hence **not A** is evaluated before the **and** term.

General recommendation is to be **generous** with parenthesis, it will make equations more readable and less prone to errors.

And you will not have to bother with precedence.

# Comments

-- In **VHDL**, when a double **dash** ( -- ) is used, any text to the right will be treated as a **comment** and will not be interpreted by the compiler.

```
--Lab 1a: Assign all switches to LEDs  
--Toggle swithces give 0 when in down position(closest to board edge)  
--LEDs are on when assign a high value  
LEDR(16 downto 0) <= SW(16 downto 0); --A comment can also be placed here.
```

“Research has shown that using lots of appropriate comments is actually a sign of high intelligence. “

*According to Mealy and Tepper, “Free range VHDL”*

# Relational operators

- equality =
- inequality /=
- Size operators < , <= , > , >=
- The operands must both be of the same type, and the result is a Boolean value (true/false)

---


Example:

```
signal a : std_logic;
```

```
.....
```

```
if a = 1 then
```

Gives an error, because *a* is  
*std\_logic*, while 1 is an *integer*





# Data type `std_ulogic` / `std_ulogic_vector`

- IEEE standards for representation of digital signals

- Available after declaration of:

```
library ieee;  
use ieee.std_logic_1164.ALL;
```

- Normally assuming values 0 and 1
- However, the desire to model three-state drivers, pull-up and pull-down outputs, high impedance state the **`std_ulogic`** type includes 9 different values

'U'	Uninitialized	
'X'	Forcing Unknown	
'0'	Forcing 0	} For synthesis of logic
'1'	Forcing 1	
'Z'	High Impedance	
'W'	Weak unknown	
'L'	Weak 0 – pull down	
'H'	Weak 1 -- pull up	
'-'	Don't care	

# Std\_logic 1164 resolution function


The sub type **std\_logic** is "resolved" **std\_ulogic**. When two or more drivers are connected together the value is determined by a "resolution table"

[illegible]


# Ex. Multiple drivers: bus

- The resolution function is used to simulate a data bus.
- Useful that the simulator can indicate an unknown value if two or more entities write to the same bus line at the same time with opposite logic values
- If one module writes to a bus, the outputs of the other module's bus line must be in tri-state (high impedance)
- The unknown value 'X' has no meaning for synthesis.

~~$y \leq 'X'$~~

 
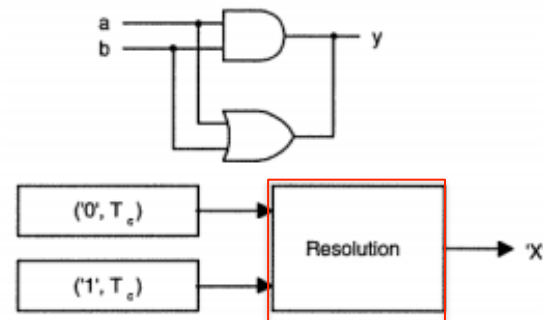
```
architecture multiply_driven_signal of my_design is
begin
    y <= a and b;
    y <= a or b;
end multiply_driven_signal;
```



Conflicting assignment must be resolved

# Description models

- Structural
  - Interconnection of components (black boxes)
  - Concurrent execution of statements
  - Can be used to create hierarchy in the code
  - Keywords: ***component*** & ***port map***
- Behavioral
  - Models how the circuit outputs will react to the circuit inputs
  - Both concurrent and sequential execution of statements
  - Keywords: ***data flow*** & ***process***

# Example of structural model

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity struct_ex is
    Port (
        A_IN   : in STD_LOGIC;
        B_IN   : in STD_LOGIC;
        C_IN   : in STD_LOGIC;
        Y_OUT  : out STD_LOGIC
    );
end struct_ex ;

architecture Structural of struct_ex is

    signal int1 : std_logic;
    signal int2 : std_logic;
    signal int3 : std_logic;

    component AND_GATE
    port (
        A, B : in  std_logic;
        Y    : out std_logic);
    end component;


    component OR_GATE
    port (
        A, B, C : in  std_logic;
        Y       : out std_logic);
    end component;

    begin

    A1: AND_GATE port map (A=>A_IN, B=>B_IN, Y=>int1);
    A2: AND_GATE port map (A=>A_IN, B=>C_IN, Y=>int2);
    A3: AND_GATE port map (A=>B_IN, B=>C_IN, Y=>int3);
    O1: OR_GATE port map (A=>int1, B=>int2, C=>int3, Y=>Y_OUT);

    end Structural;
```

 **Can not directly connect together  
the input/output of a component to  
another component's output/input!  
Must use an internal signal (such as  
int1 in this example), unless a  
connection to a port is made**



# Behavioral model styles

- Non-procedural (Data-flow)
  - Concurrent execution
- Procedural (more in next lecture)
  - Algorithmic
    - step-by-step calculations / sequence of operations
  - Sequential execution of statements within process
  - Execution of a process is equivalent to a single concurrent statement.
- All VHDL processes execute concurrently


# Data flow (non-procedural)

- Concurrent statements
  - Executed in parallel (order or statements is irrelevant)
- Event driven
  - Executed only if transition/change on input

-----  
B <= C; --executed if transition on C  
A <= B; --executed if transition on B

is equivalent to

A <= B;  
B <= C;  
-----

 

# Data flow (non-procedural)

```
architecture CONCURRENT of MULTIPLE is
    signal Z, A, B, C, D : std_logic;
begin
    Z <= A and B;
    Z <= C and D;
end CONCURRENT;
```

Multiple drivers for one signal

Conflicting assignment must be resolved



# Code structure

```
Architecture rtl of ex is
```

```
Parallell deklarasjonsdel
```

```
begin
```

```
.....  
Parallell VHDL
```

```
.....  
Process (...)
```

```
Sekvensiell deklarasjonsdel
```

```
begin
```

```
.....  
Sekvensiell VHDL
```

```
end process;
```




```
.....  
Parallell VHDL
```

```
end rtl;
```

Process  
parallelt  
VHDL  
kommando

Parallell  
del

# Ex.: 7-segment decoder

  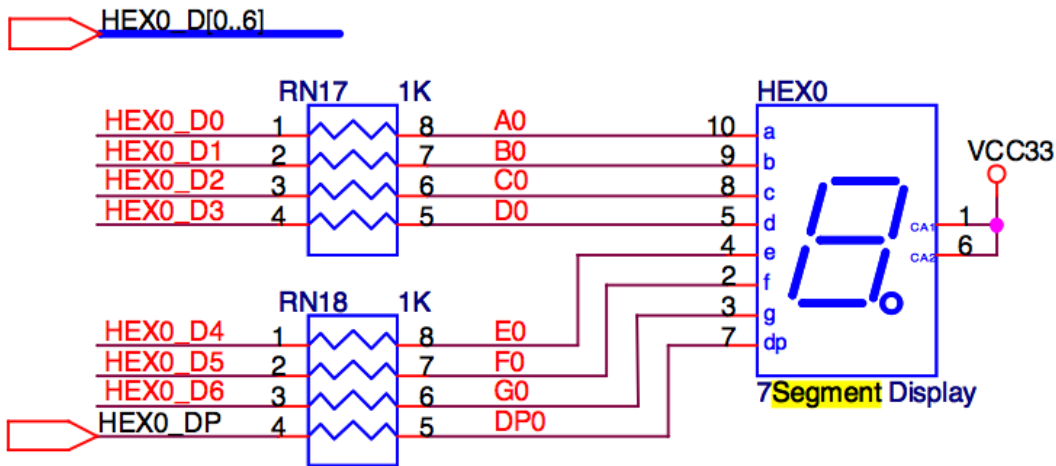

			0	1	2	3	4	5	6
Digit	gfedcba	abcdefg	a	b	c	d	e	f	g
0	0x3F	0x7E	on	on	on	on	on	on	off
1	0x06	0x30	off	on	on	off	off	off	off
2	0x5B	0x6D	on	on	off	on	on	off	on
3	0x4F	0x79	on	on	on	on	off	off	on
4	0x66	0x33	off	on	on	off	off	on	on
5	0x6D	0x5B	on	off	on	on	off	on	on
6	0x7D	0x5F	on	off	on	on	on	on	on
7	0x07	0x70	on	on	on	off	off	off	off
8	0x7F	0x7F	on	on	on	on	on	on	on
9	0x6F	0x7B	on	on	on	on	off	on	on
A	0x77	0x77	on	on	on	off	on	on	on
b	0x7C	0x1F	off	off	on	on	on	on	on
C	0x39	0x4E	on	off	off	on	on	on	off
d	0x5E	0x3D	off	on	on	on	on	off	on
E	0x79	0x4F	on	off	off	on	on	on	on
F	0x71	0x47	on	off	off	off	on	on	on

'0' → ON

'1' → OFF

# Ex.: 7-segment decoder

```
HEX1(6) <= ((not A) and (not B) and (not C)) or ((not A) and B and C and D) or  
(A and B and (not C) and (not D)); --g
```

```
HEX1(5) <= ((not A) and C and D) or ((not A) and (not B) and D) or  
((not A) and (not B) and C) or (A and B and (not C) and D); --f
```

```
HEX1(4) <= ((not A) and D) or ((not B) and (not C) and D) or  
((not A) and B and (not C)); --e
```

```
HEX1(3) <= (B and C and D) or ((not A) and (not B) and (not C) and D) or  
((not A) and B and (not C) and (not D)) or (A and (not B) and C and (not D)); --d
```

```
HEX1(2) <= (A and B and C) or (A and B and (not D)) or  
((not A) and (not B) and C and (not D)); --c
```

```
HEX1(1) <= (A and C and D) or (B and C and (not D)) or  
(A and B and (not D)) or ((not A) and B and (not C) and D); --b
```

```
HEX1(0) <= ((not A) and (not B) and (not C) and D) or ((not A) and B and (not C) and (not D)) or  
(A and B and (not C) and D) or (A and (not B) and C and D); --a
```

The use of logical operators and concurrent signal assignment is no longer comfortable.

# VDHL

Non-procedural (data-flow)	Procedural (sequential)
<ul style="list-style-type: none"><li>• <b>Process statement</b></li><li>• <b>When else statement</b></li><li>• <b>With select statement</b></li><li>• <b>Signal declaration</b></li><li>• Block statement</li></ul>	<ul style="list-style-type: none"><li>• <b>If- then- else statement</b></li><li>• <b>Case statement</b></li><li>• <b>Variable declaration</b></li><li>• <b>Variable assignment</b></li><li>• Loop statement</li><li>• Return statement</li><li>• Null statement</li><li>• Wait statement</li></ul>
Allowed in both non-procedural and procedural part	
<ul style="list-style-type: none"><li>• <b>Signal assignment</b></li><li>• <b>Declaration of types and constants</b></li><li>• Function and procedure calls</li><li>• Assert statements</li></ul>	

# When-else / with-select (non-procedural)

## Conditional signal assignment

general format:

*expression* when *condition* else  
*expression* when *condition* else  
*expression* **when others**;

example:

Z <= A when S = "00" else  
B when S = "11" else  
C;

## Selected signal assignment

general format:


with *selection* select  
*expression* when *condition*,  
*expression* when *condition*,  
*expression* when others;

example:

with S select  
Z <= A when "00",  
B when "11",  
C when others;
 
# Ex. *when – else*: Tri-state buffer

- The output buffer can be put into a high impedance ('Z') state, such that only one entity writes to the bus
  - Three possible signal levels: '0', '1', 'Z'
- FPGAs and CPLDs have three-state buffers on the outputs (the signals defined as **port** in the entity)
- However, many programmable logic devices can not have three-state buffers internally on the circuit (on internal signals)




When – else

`Data_bus <= data when enable = '1' else (others => 'Z');`

```
Data_bus : inout std_logic_vector(7 downto 0));
```

# Ex. *when – else*: Tri-state buffer

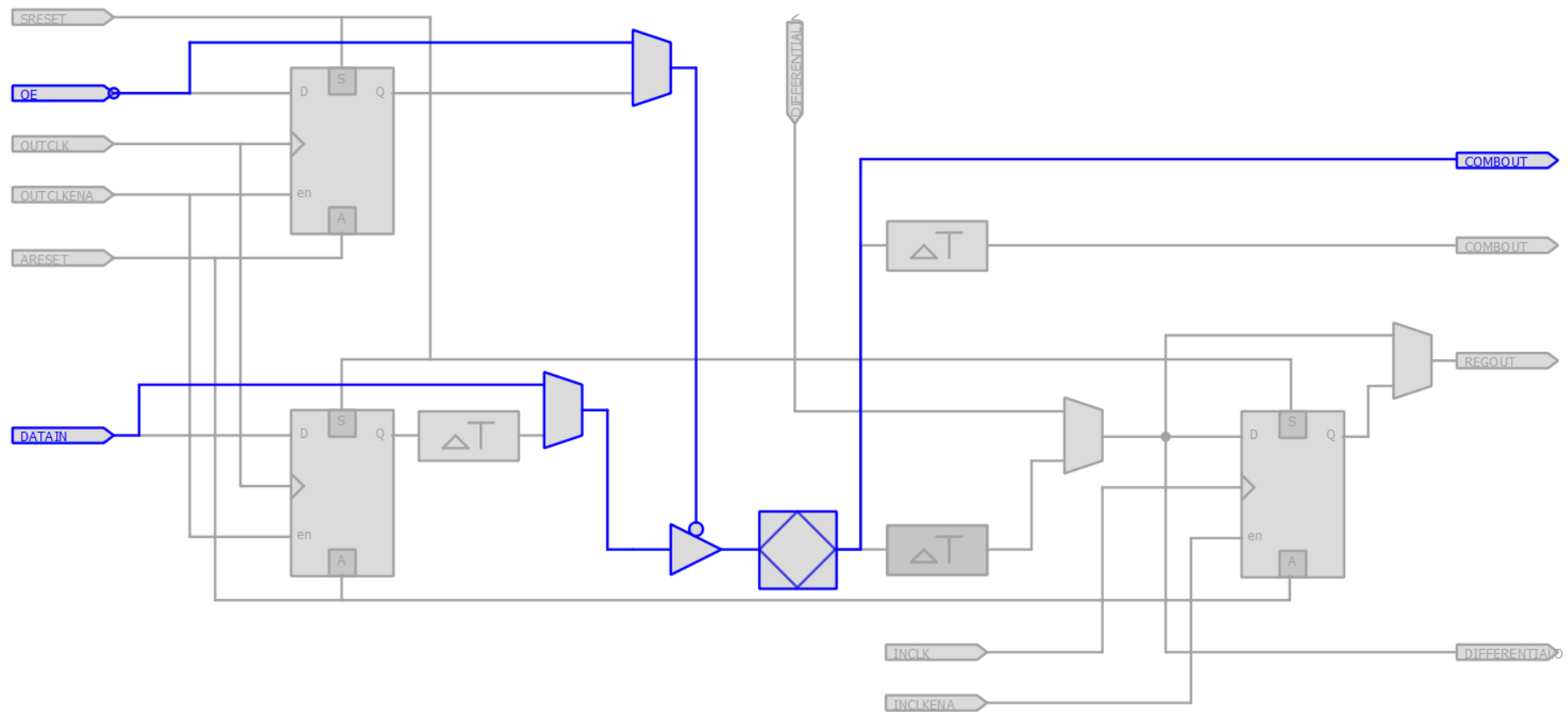


# Ex.: 7-segment decoder

```
with SW(3 downto 0) select
  HEX0 <= "1000000" when "0000",      --0
  "1111001"      when "0001",      --1
  "0100100"      when "0010",      --2
  "0110000"      when "0011",      --3
  "0011001"      when "0100",      --4
  "0010010"      when "0101",      --5
  "0000010"      when "0110",      --6
  "1111000"      when "0111",      --7
  "0000000"      when "1000",      --8
  "0010000"      when "1001",      --9
  "0001000"      when "1010",      --A
  "0000011"      when "1011",      --b
  "1000110"      when "1100",      --C
  "0100001"      when "1101",      --d
  "0000110"      when "1110",      --E
  "0001110"      when "1111",      --F
  "1111111"      when others;
```



# DE1-SoC board

 


User Manual: [DE1-SoC User Manual\(rev.C/rev.D Board\)](#)

TERASIC: [DE1-SoC webpage](#)

# DE1-SoC board revisions

rev. D

 

## What are the parts changed?

The JTAG chain has been changed. Starting from rev. C, the HPS comes before FPGA in the JTAG chain. This is to bypass a bug in the DS-5 where reset can't function properly.


## DE1-SoC

[Overview](#) [Specification](#) [Layout](#) [Resources](#) [Compare](#) [Demo](#) [Kit Contents](#) [Order Now](#)

 
## DE1-SoC Board

[Like](#) 171 people like this.

rev. B JTAG chain: USB Blaster II → FPGA → HPS → USB Blaster II



 JTAG chain starting from rev. C: USB Blaster II → HPS → FPGA → USB Blaster II




[How to distinguish rev. B, rev. C, rev. D, rev. E and rev. F board?](#)

## Documents



Title	Version	Size(KB)	Date Added	Download
DE1-SoC User Manual(rev.E Board)	1.2.3	7598	2015-08-06	<a href="#">PDF</a>
DE1-SoC User Manual (rev.F Board)	2.0.1	7787	2015-08-06	<a href="#">PDF</a>
DE1-SoC User Manual(rev.C/rev.D Board)	1.2.2	6472	2015-04-07	<a href="#">PDF</a>
DE1-SoC User Manual(rev.B Board)	1.0	9830	2014-02-07	<a href="#">PDF</a>
DE1-SoC Learning Roadmap	1.0	2079	2014-02-07	<a href="#">PDF</a>

# DE1-SoC board

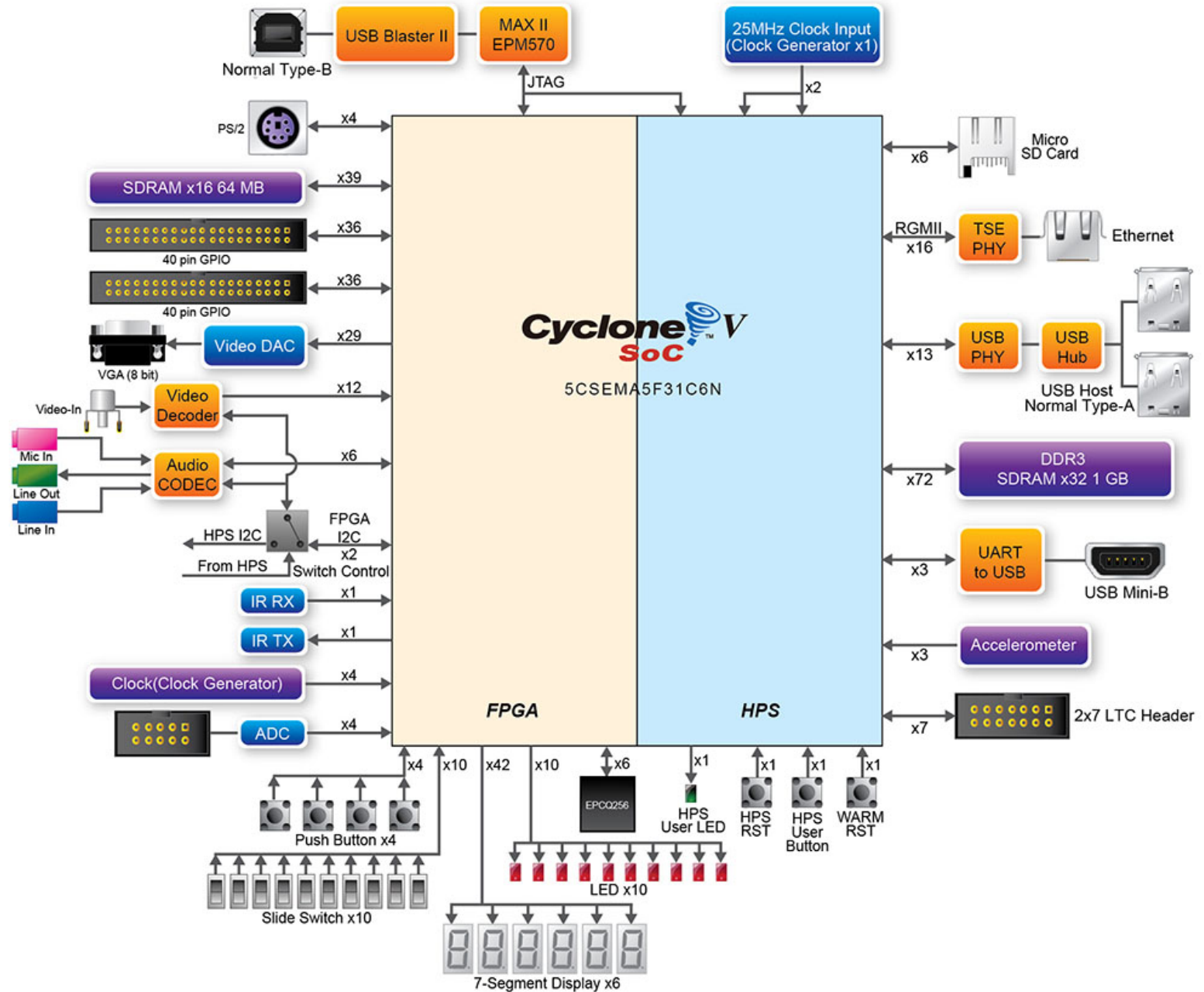




# Design using FPGA/CPLD

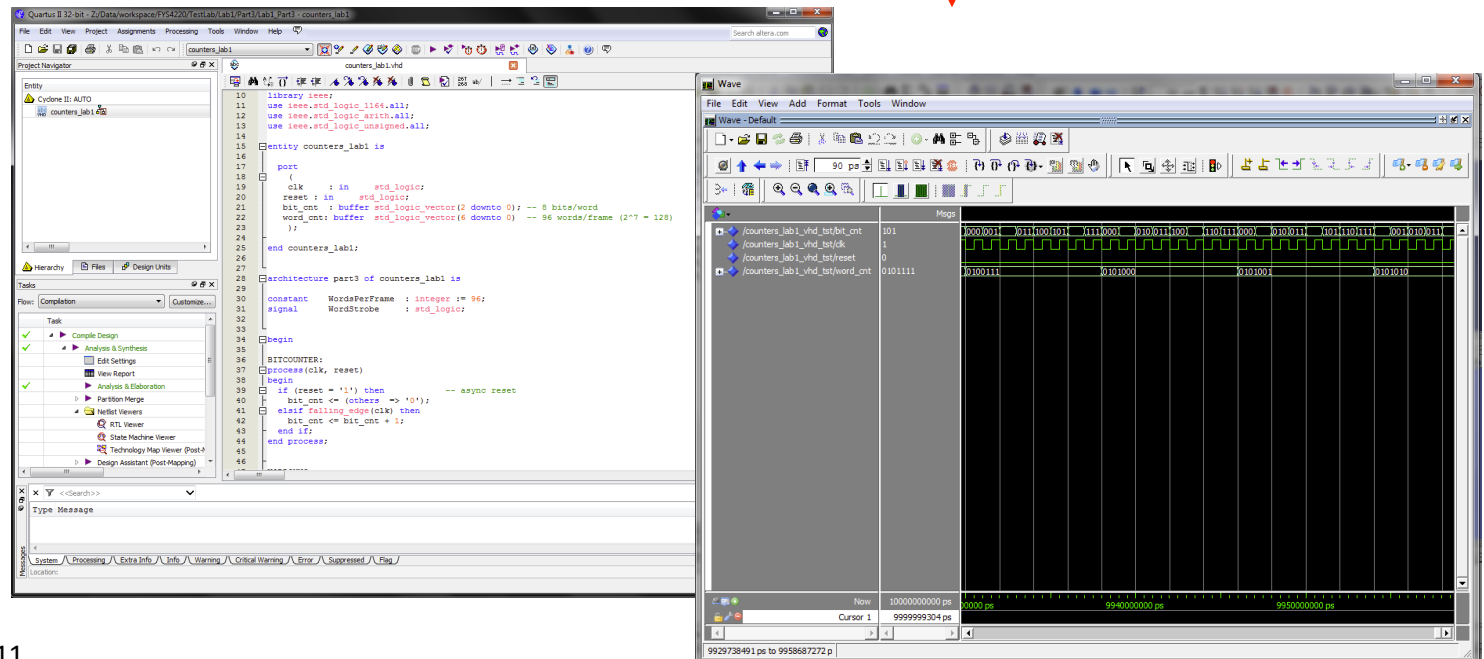 

# Quartus II Development software

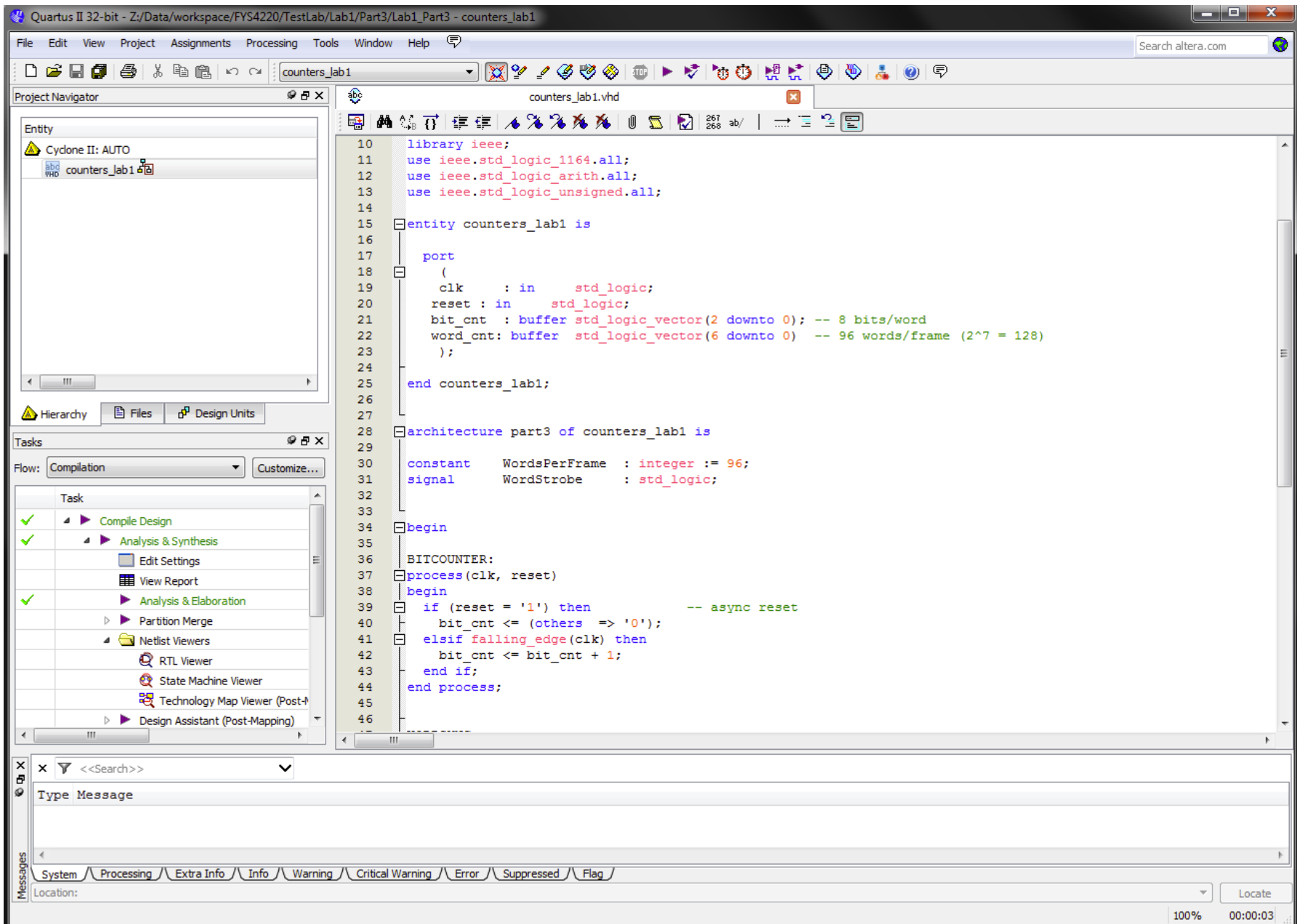

# Quartus system integration tool (QSYS)

Qsys - ucoscpcu.qsys (Z:\workspace\GIT\projects\FYS4220-tests\uCosII\test\qsys\ucoscpcu.qsys)

File Edit System View Tools Help

Component Library

Project

- New Component...
- System

Library

- Bridges
- Clock and Reset
- Configuration & Programming
- DSP
- Embedded Processors
- Interface Protocols
- Memories and Memory Controllers
- Merlin Components
- Microcontroller Peripherals
- Peripherals
- PLL
- Qsys Interconnect
- Verification
- Window Bridge

System Contents

Use	Connections	Name	Description	Export	Clock	Base	End	IRQ	Op
<input checked="" type="checkbox"/>		<b>clk</b> clk_in clk_in_reset clk clk_reset	Clock Source Clock Input Reset Input Clock Output Reset Output	<b>clk</b> <b>reset</b> Double-click to export Double-click to export	clk				
<input checked="" type="checkbox"/>		<b>cpu</b> clk reset_n data_master instruction_master jtag_debug_module_re... jtag_debug_module custom_instruction_m...	Nios II Processor Clock Input Reset Input Avalon Memory Mapped Master Avalon Memory Mapped Master Reset Output Avalon Memory Mapped Slave Custom Instruction Master	Double-click to export Double-click to export Double-click to export Double-click to export Double-click to export Double-click to export Double-click to export	clk [clk] [clk] [clk] [clk] [clk]		IRQ 0	IRQ 31	
<input checked="" type="checkbox"/>		<b>onchipmem</b> clk1 s1 reset1	On-Chip Memory (RAM or ROM) Clock Input Avalon Memory Mapped Slave Reset Input	Double-click to export Double-click to export Double-click to export	clk [clk1] [clk1]	0x0804_0800	0x0804_0fff		
<input checked="" type="checkbox"/>		<b>sysid</b> clk reset control_slave	System ID Peripheral Clock Input Reset Input Avalon Memory Mapped Slave	Double-click to export Double-click to export Double-click to export	clk [clk] [clk]	0x0804_1098	0x0804_109f		
<input checked="" type="checkbox"/>		<b>jtag_uart</b> clk reset avalon_jtag_slave	JTAG UART Clock Input Reset Input Avalon Memory Mapped Slave	Double-click to export Double-click to export Double-click to export	clk [clk] [clk]	0x0804_1090	0x0804_1097		
<input checked="" type="checkbox"/>		<b>timer</b> clk reset s1	Interval Timer Clock Input Reset Input Avalon Memory Mapped Slave	Double-click to export Double-click to export Double-click to export	clk [clk] [clk]	0x0804_1020	0x0804_103f		
<input checked="" type="checkbox"/>		<b>led</b> clk reset s1 external_connection	PIO (Parallel I/O) Clock Input Reset Input Avalon Memory Mapped Slave Conduit	Double-click to export Double-click to export Double-click to export <b>led_external_connection</b>	clk [clk] [clk]	0x0804_1070	0x0804_107f		
<input checked="" type="checkbox"/>		<b>sdram</b> clk reset s1 wire	SDRAM Controller Clock Input Reset Input Avalon Memory Mapped Slave Conduit	Double-click to export Double-click to export Double-click to export <b>sdram_wire</b>	clk [clk] [clk]	0x0400_0000	0x07ff_ffff		
<input checked="" type="checkbox"/>		<b>lcd</b> reset clk control_slave external	Altera Avalon LCD 16207 Reset Input Clock Input Avalon Memory Mapped Slave Conduit	Double-click to export Double-click to export Double-click to export <b>lcd_external</b>	[clk] clk [clk]	0x0804_1060	0x0804_106f		

Messages

Description

Path

2 Info Messages


0 Errors, 0 Warnings

# Development software

- Quartus II Web Edition and Modelsim-Altera Starter Edition software can be downloaded for free from the [Altera web page](#)
- Contains also QSYS and NIOSII EDS
- Latest version is v15.0 (14.0 installed in lab.)
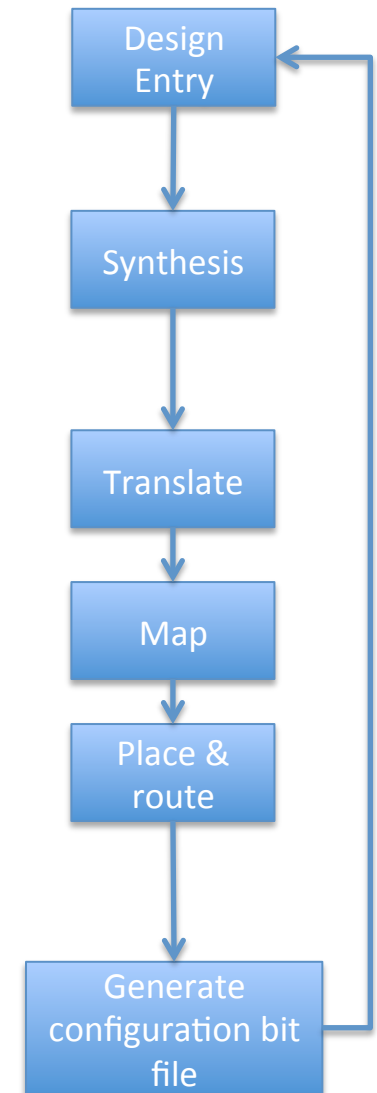
# General design flow steps


- Design entry
  - Register Transfer Level (RTL) description of design (schematic or HDL)
- Synthesis
  - Checks code syntax, converts abstract form of desired circuit behavior into a design implementation of basic gate level primitives (netlist), i.e. circuit logic elements (gates, flip-flops, etc). A netlist is a text-based representation of a logic diagram.
- Translate
  - Merges netlist and constraints (e.g. physical port assignment, timing) into device specific design file.
- Map
  - Fits the design into specific device resources (LUT, FF, RAM etc)
- Place and route
  - Decides where in the die the resources will be placed and wires them together (accounts for timing constraints)
- Generate configuration bit file
  - That can be downloaded to the FPGA





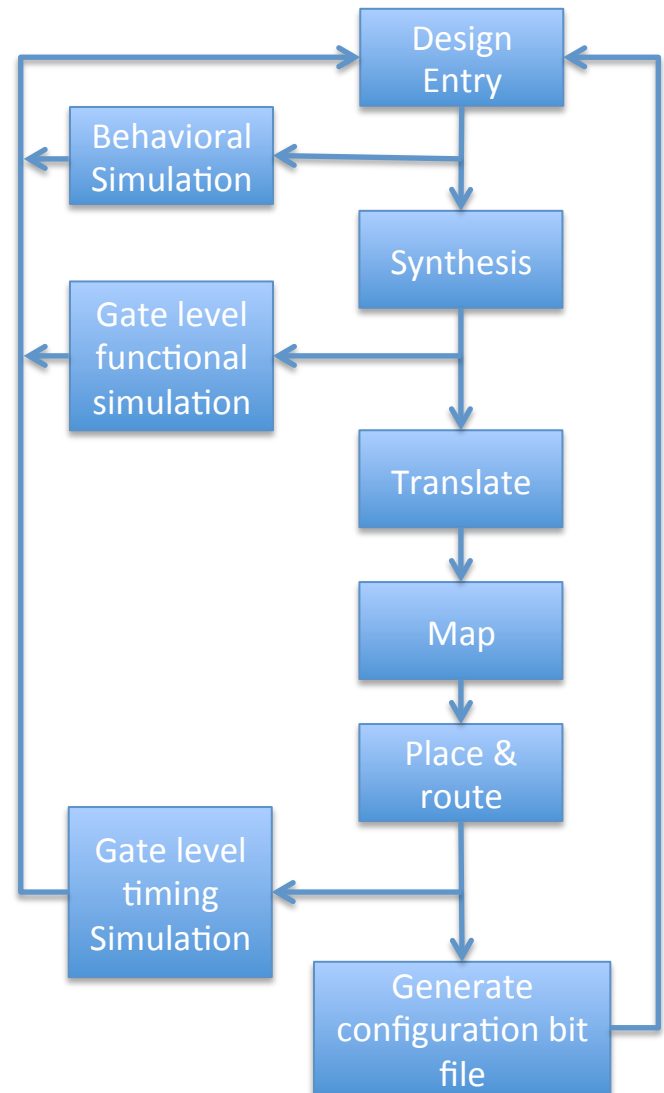
# General simulation steps

- Behavioral simulation
  - Simulation to verify RTL behavioral code (no timing and resource information)
- Gate level functional simulation
  - Run simulation on gate level description generated by the synthesizer.
  - Can discover improper coding that works at RTL level but which violates synthesis coding conventions.
    - E.g. omitting a signal in the sensitivity list.
- Gate level timing simulation
  - Gate level simulation with propagation delays





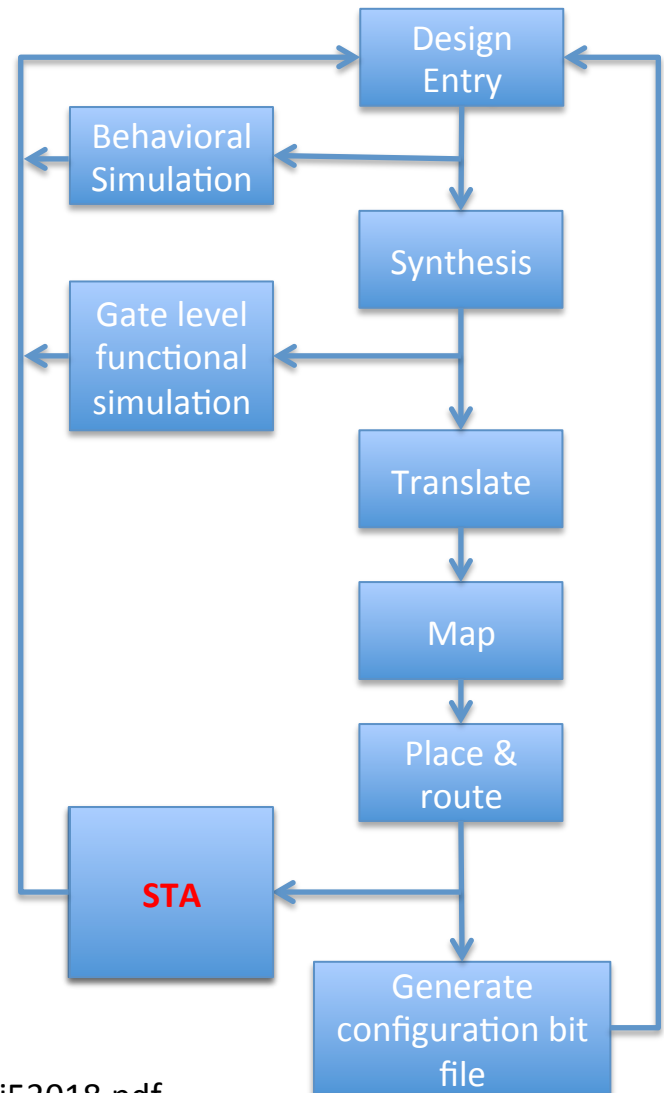
# Static Timing Analysis

- Gate level timing simulation of an entire design can be slow and should be avoided.
- In fact, not supported for Cyclone/Arria/Stratix V devices.
- Instead, use Static Timing Analysis (STA)
  - method of computing the expected timing of a digital circuit without requiring simulation
  - Considers timing of paths from e.g. **register to register, input port to register, register to output port, purely combinational paths**.
  - No need for test vectors
  - However, does not check functionality of design.  
=> combine STA with behavioral simulation (RTL).



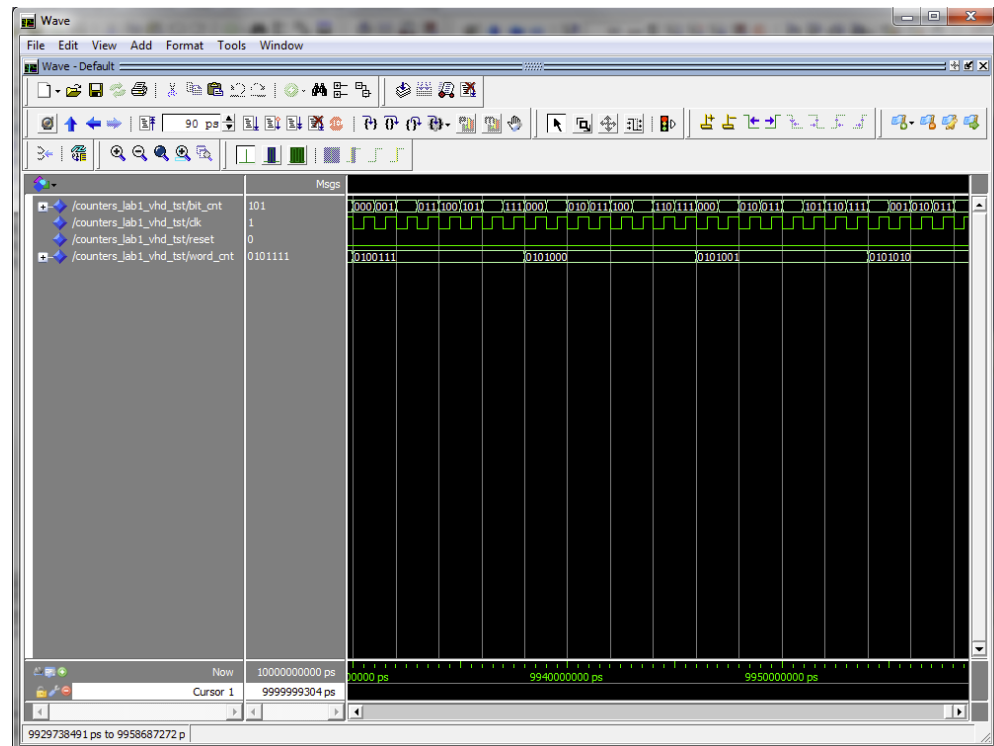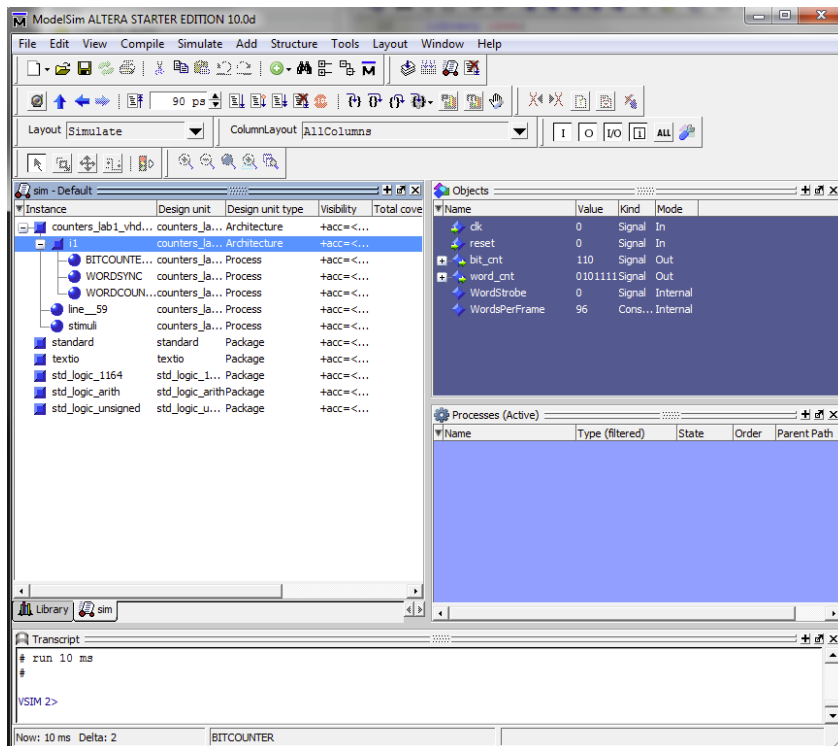
 
# How to simulate VHDL code

- Use a simulation tool like e.g. ModelSim
- Test bench to apply stimuli/test inputs to the VHDL code
- Visual inspection through graphical output (waveform)
- Self-checking test benches (add code to check and verify result)


  
# Why focus on Verification

Consider a) **FPGA development and**  
b) **Further work related to FPGA quality**



Average Design & Functional  
Verification tasks  
- as seen in some reasonably  
structured projects.

# Room V442, 4<sup>th</sup> floor of Physics building





# Please keep the lab. Clean and tidy



DE1-SoC boards

