

EE 101 Lab 1 – Sound the Alarm

1 Introduction

In this lab you will design, implement and then test a simple logic circuit emulating a home alarm system. You will use the Digital Trainer board for this lab and may work in teams of two, turning in one answer sheet for the both of you.

2 What you will learn

This lab is intended to teach you the basics of building and wiring digital circuits. You will also be asked to think of a test strategy to ensure your circuit works as specified in the following English-language description.

3 Background Information and Notes

The Alarm System: The alarm system to be designed has the following inputs.

Input	Description
N	The system enable (i.e. the on/off state of the alarm system). 1 = Enabled / 0 = Disabled)
W	Window sensors = 1 indicates all windows are secured/closed
D	Door sensors = 1 indicates all doors are secured/closed
G	Garage sensor = 1 indicates the garage door is secure
X	Exiting input. 1 indicates that you are currently leaving the house and thus an open door or window should not cause the alarm to turn on. 0 indicates that you are out of the house.

The only output of the alarm system should be a single bit, A, which will be 1 if the alarm is activated and 0 otherwise. **The alarm should activate if the system is enabled, you are not exiting, and the house is not secure. The house is considered secure if all the sensors (windows, doors, garage) are 1.**

Implementation: For this lab you will implement your design on the provided Digital Trainer Board. Read the Digital Trainer board user manual and/or follow along as your instructor describes the features and operation of the board. Some important do's and don'ts will be highlighted.

4 Prelab

None

5 Procedure

- Given the description of the alarm system in section 3, design a logic circuit to implement the alarm system. Use only inverters and the 2-input AND and OR gates (no NOR and NAND for now). For inputs and outputs use the following mapping:

Logical Input/Output	Trainer Board I/O Device
N	SW1
X	SW4
W	PB1
D	PB2
G	PB3
A	LED5

Since the push buttons (PB1-PB3) output a 1 by default this means the window, door, and garage values are *secure* by default. When we press the buttons it will produce a '0' indicating someone has opened or broken the window, door or garage. This is reiterated in Figure 1.

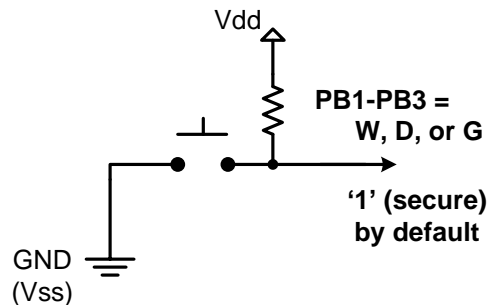


Figure 1 - PB outputs producing the W, D, and G values

When implementing your circuit, note that you only have 2-input gates available. However, you should be able to easily handle this shortcoming by manipulating your design slightly (think about how you could construct a 3-input AND gate using two 2-input AND gates.)

- Once you have wired your design, it is now time to test it and make sure it is correct. To test this circuit exhaustively would require trying every possible input combination and ensure the output is as expected. How many combinations would this approach require? Instead, use your understanding of the intended logic design to devise a list of input combinations (a.k.a. test vectors) that provide high satisfaction that your design is operating correctly (e.g. $\{N, X, W, D, G\} \Rightarrow A = \{0, 0, 0, 0, 1\} \Rightarrow 0$, $\{1, 0, 0, 1, 0\} \Rightarrow 1, \dots$). Use the attached table on page 4 to list your (near) minimal number of combinations, the

expected value of A and the actual value of A produced by your circuit when you plug in the given combination. If you find mismatches between your expected and actual outputs, go back to your circuit and make sure you've implemented it correctly.

Hint: At the very least we need to prove the alarm is off under normal conditions but also turns on under all the necessary cases. Think about the gate types you are using and how each input should affect the output (e.g. an OR gate should output '1' when only a single input is '1' even if all other inputs are '0'). Somewhere around six to eight combinations (vectors) should suffice.

6 Review

1. How many combinations would be necessary to exhaustively test your design?
2. Provide a short justification (a paragraph) explaining how you chose your minimal set of test vectors and why they provide a high degree of satisfaction that your design works under all conditions.

7 Lab Report

Name: _____ Score: _____

Due: _____

(Detach and turn this sheet along with any other requested work or printouts)

Turn in the following items:

1. Original schematic of your working design.

2. Instructor Signoff of working design: _____

Continued on next page.

8 EE 101 Lab 1 Grading Rubric

Name(s): _____ Score: _____ / 100

Req. / Guideline	Mult	Score	10 (Excellent)	8 (Good)	5 (Average)	2 (Poor)	(0) Failure
Schematic Design	3		Correct Logic with near-minimal number of gates	Correct logic but with non-minimal number of gates	Slight error in logic affecting only 1 or 2 input cases	Major error in logic	Missing
Test Vectors	4		Near minimal number of vectors to sufficiently test logic	Too many vectors but logic is sufficiently tested	Near minimal number of vectors but does not sufficiently test logic	Vectors chosen haphazardly	Missing
Review Q1	1		Correct		Near correct	Wrong	Missing
Review Q2	2		Demonstrates clear understanding and correct reasoning	Demonstrates reasonable understanding and correct reasoning	Demonstrates some understanding with adequate reasoning	Demonstrates little understand or poorly reasoned	Missing
Late			-10 per day				
TOTAL							