

Exp. 4. USE OF BASIC ELECTRONIC MEASURING INSTRUMENTS, Part III

PURPOSE:

- To become familiar with more of the instruments in the laboratory.
- To become aware of operating limitations of input and output devices.
- To understand the influence of instruments on circuits (*Loading effect*)
- To understand and be able to measure the internal impedance of function generator and oscilloscope.
- To understand the impact of interference signals and shielding on current and voltage readings.

This experiment relates to the following **learning objectives** of the course

1. Ability to interconnect equipment and devices such as multimeter, counters, and oscilloscope to achieve required results.
2. Ability to relate practical laboratory results with lecture theory.
3. Ability to analyze and evaluate data.

LAB EQUIPMENT

- Decade Resistance Boxes
- [Agilent E3640A DC Power Supply](#)
- [Agilent 34410A Digital Multimeter/Timer/Counter](#)
- [Agilent 33120A Function Generator \(FG\)](#)
- [Agilent 54621A Oscilloscope](#)¹
- [Triplett 630 Analog Multimeter](#)

STUDENT PROVIDED EQUIPMENT:

- 2 BNC to double-banana leads
- 6 Banana-to-banana leads

Experiment Sections:

- 1) Internal Impedance of the Function Generator and Oscilloscope
- 2) Loading Effects
- 3) Interference Signals
- 4) Ground Loops

Section 1) Internal Impedance of the Function Generator and the Oscilloscope

Overview of the influence of instruments on circuits (*Loading effect*)¹


Any instrument which accepts input signals will require both a voltage and a current to allow it to detect a signal. This is because every signal must convey some energy/power—except the trivial case of the signal “0 volts.” When an input voltage is applied to, say, an oscilloscope, it must also draw a small current to allow it to recognize that a signal has arrived. The amount of current required by an instrument depends upon how it has been designed and built. The better an instrument (e.g., a scope or a multimeter) is, the smaller the current it needs to register a given voltage or current, i.e., the higher its input resistance.

¹ Partially adopted and edited in part from “Internal Impedance of Instruments,” courtesy of NJIT ECE department

In the previous experiments, we built circuits and made measurements by attaching instruments (a multimeter or a scope) to various circuit points. In analyzing the circuits' performance, we neglected the instruments' presence assuming that they have no influence on current and voltage distributions. Such an assumption is valid only for "ideal" instruments but may be quite reasonable also for actual instruments in most practical cases. There are situations, however, where the presence of an instrument attached to a circuit alters its performance to the point where the measurement is meaningless, and other methods of circuit evaluation are needed. For instance, if a voltmeter connected across a circuit element draws a current comparable to the current flowing through that element, it can change the current and voltage distribution in the rest of the circuit. An ideal voltmeter does not draw any current, a good voltmeter very little. Modern digital voltmeters approximate the ideal case in this respect.

An instrument, such as a digital or analog voltmeter, may be represented by an equivalent circuit consisting of an ideal meter and its internal resistance. More generally, we should consider internal impedance, which besides resistance may have a capacitive or inductive component. For example, the capacitive component of the scope input impedance plays a role in high-frequency measurements.

Another class of instruments in which internal resistance (ignoring the frequency dependence for now) plays an important role is represented by power supplies. A voltage supply, such as a battery or power supply can be represented as an ideal voltage source and a series resistance (output resistance). In an ideal voltage source, this resistance is zero; there is no voltage drop across it, and the output voltage is independent of the amount of the current drawn. The Agilent function generator is an output device with an output resistance of 50Ω . To account for the loading effect, the function generator has a "High Z" and " 50Ω " setting for output termination as described in the figure below.

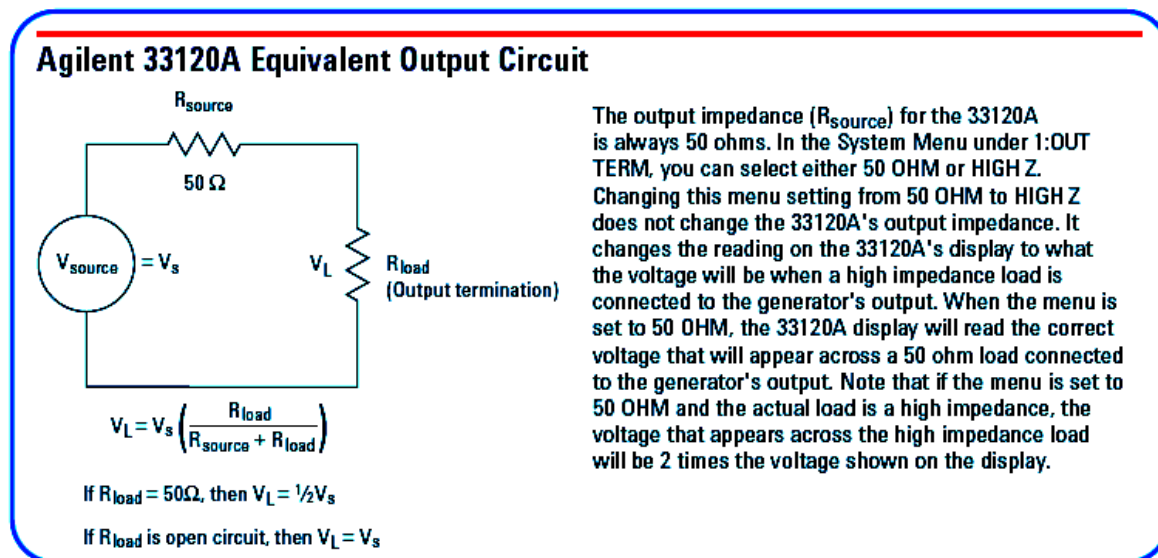


Source: <http://www.hit.bme.hu/~papay/edu/Acrobat/HP33120A.pdf>

In this section, the internal resistance of basic instruments used in the laboratory will be measured and situations where their internal resistance plays an important role will be explored. The lesson is worth remembering whenever external instruments are connected to an electronic circuit. We will measure the input impedance for our most important instrument, the oscilloscope, in this laboratory experiment. For now, we ignore the frequency dependence of the oscilloscope's impedance. The complex impedance of the oscilloscope requires knowledge of RC-circuits response, which you may not have covered in lecture yet.

Internal impedance of the Function Generator and the Oscilloscope.

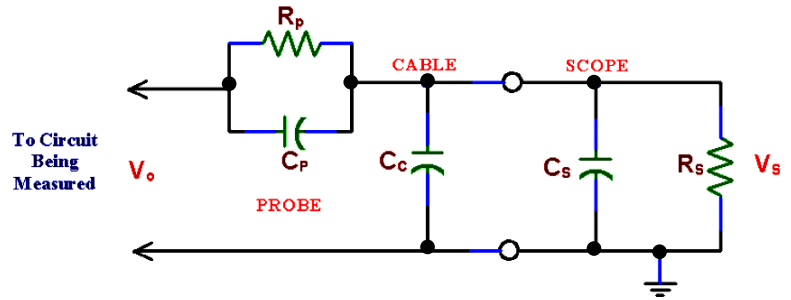The input impedance of an oscilloscope is a complex quantity which can be represented by a resistance in parallel with a capacitance between the scope input terminals and ground. The impedance is thus frequency dependent. To compensate for this frequency dependence, scope probes are used. The circuit representing an oscilloscope and probe is shown in the figure.




The circuit representing an oscilloscope with a probe

R_s -scope internal resistance, C_s -scope internal capacitance, C_c - cable capacitance, R_p - probe resistance, C_p - probe capacitance

For DC measurements only, we can consider the scope's input impedance as being resistive. For AC measurement, we must consider the scope's input impedance since it contains an internal capacitive component (*frequency dependent*). Note that the capacitance of the scope cable adds to the internal shunt capacitance of the scope input. The scope probe eliminates the effects of this capacitance by compensating it with another capacitance (*scope probe capacitance*). The probe capacitance is chosen so that the measurement is independent of frequency. Thus, assuming the probe has effectively eliminated the frequency dependence of the scope, we can obtain the scope internal resistance instead of its internal impedance via the same simple technique we use to find the internal impedance of a multimeter.


Note: throughout this experiment, set the Agilent multimeter to "autorange" on the AC scale

- Place the FG output termination to "HIGH Z" (Menu -> SYS -> 1. OUT TERM -> HIGH Z, then enter); this will allow the FG reading to reflect the multimeter reading for the open circuit voltage measurement. Configure the FG to supply a 4.0 V_{rms} sine wave @ 400 Hz with 0V DC offset. Measure and record the output with the multimeter.
- Connect the FG outputs to a decade box resistor (with a 1-Ω/step resolution) as shown below.

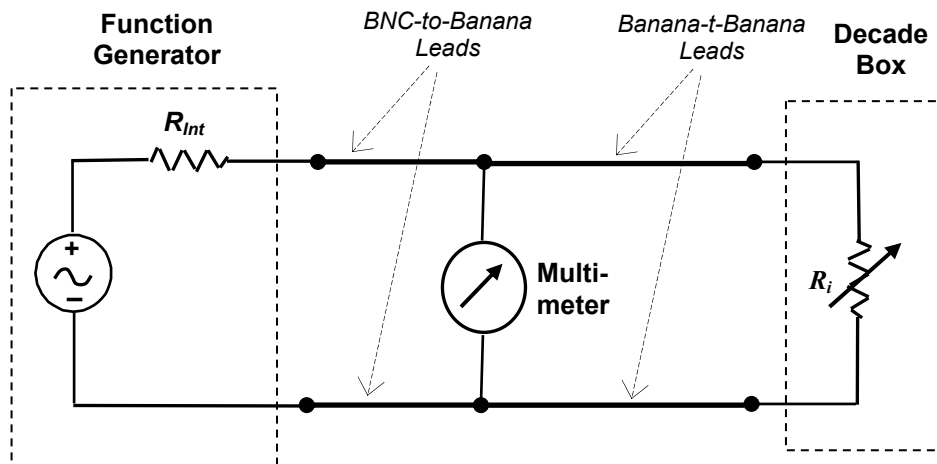

- c) Adjust the resistance dials on the decade box until the output voltage of the FG, as measured by the Agilent multimeter, at the terminals of the decade box, is one half of the FG's original voltage setting.
- d) Disconnect the decade box. Measure the resistance of the decade box and record this value.
- e) Record the resistance of the BNC-to-banana cable, then subtract it from your resistance measure in part d (which includes the resistance of the banana-to-banana cables) leads and subtract them from the measured resistance of the decade box. This gives the internal resistance (*output resistance*) of the Function Generator. Explain why.

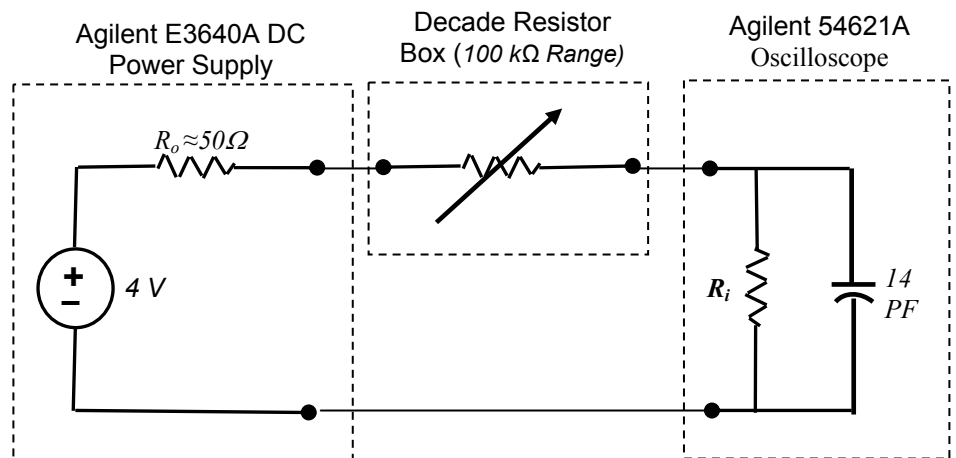- f) Obtain the internal resistance of the Agilent scope by setting up the circuit shown. Note that for DC signals, the internal capacitance of the scope behaves as an open. For this experiment, do not use the scope probes. Otherwise the internal resistance of the probes (9 M Ω) would have to be included in the circuit and hence you would not be able to obtain the scope's internal resistance as described here.



Use BNC-to-banana leads instead of scope probes. For your calculation, use the nominal value of the Agilent DC power supply output impedance ($R_o \approx 50\Omega$) (Note that the output impedance of the power supply could be found as was done for the function generator). To find the scope's internal resistance R_i , select the resistance of the decade box which causes the voltage as observed on the scope to drop to 1/2 of the voltage measured directly (without the decade box). For DC measurement using scope, you can use its "Quick Meas" and "Average" setting. If necessary, use two decade boxes in series (with different ranges) to obtain precise readings. Make sure to use the oscilloscope for the two DC measurements (with and without the resistor) and do not forget to subtract the 50 Ω output resistance of the power supply from the decade box reading to determine the scope's internal resistance. Record the measured internal resistance of the scope. Also, since the type of input coupling to the oscilloscope matters here, state which one (AC or DC) you used.

Note: In addition to using Quick Measure > Averaging—which calculate the average of *each* scope trace—press Acquire > Averaging and set # Avgs to its maximum, thereby averaging over several traces. As you will see, this will eliminate the random fluctuations from the signal, leaving mainly the DC output of the supply. Note that each time you change the resistance of the decade box, you should retrigger the scope (by pressing Run/Stop twice) to restart the trace-averaging process

Questions: Section 1

- 1) Use the FG user's manual to determine the internal impedance specification. Does this value agree with your measured value? Calculate a percent difference between the two values.
- 2) Once again, explain the possible consequences of setting the voltage before or after connecting the supply to the circuit in terms of the internal impedance of the input device. A circuit diagram would help here.

- 3) Explain why the scope's internal resistance is equal to the decade box reading, minus the DC source output resistance, when the voltage drops to half the original value. Neglect the resistance the meter leads in this question.
- 4) Compare the measured value of the internal resistance of the scope with the manufacturer's nominal value. Record the percent difference.

Section 2) Loading Effects

- a) Use the same FG output as Section 1, 3.0 V_{rms} sine wave @ 400 Hz with 0V DC offset.

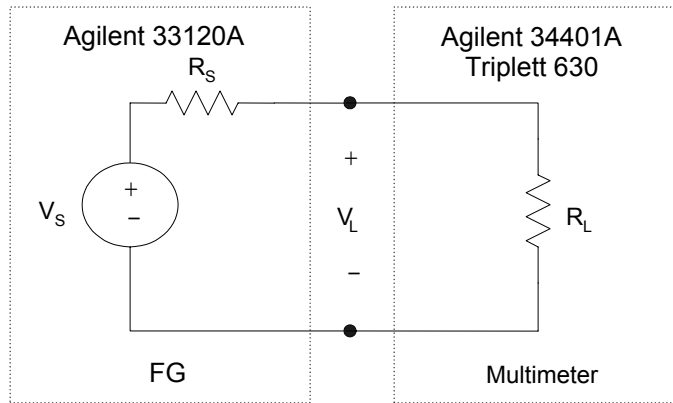


Fig. 1 Equivalent Circuit for Section 2 Parts (b), and (c).

- b) With the Agilent Multimeter, measure and record both the DC and AC values of the waveform. Note when you measure an AC signal with zero DC offset, the digital reading of the Agilent multimeter (set to DC) fluctuates around zero.
- c) Using the Triplet 630, measure and record both the DC and AC values of the waveform. Be sure to zero the Triplet analog meter before using it. Also, for all AC measurements with Triplet meter in this section, use the 12 V scale. (You will see why the choice of scale is significant in the Questions)
- d) Set the decade box resistance to 10k Ω . Place it in series with the FG and the Agilent multimeter (set on the AC voltage scale). Record the voltage reading in your lab notebook. **Note:** This is not the usual way to use a voltmeter.
- e) Repeat d) using the Triplet 630

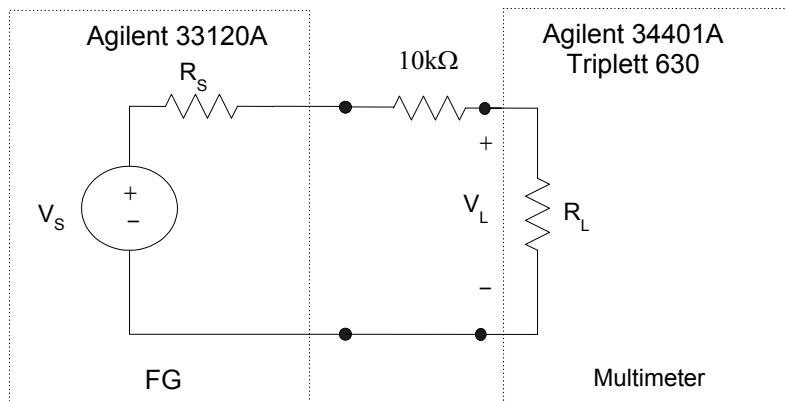


Fig. 2 Equivalent Circuit for Section 2 Parts (d) and (e).

Questions: Section 2

- 1) From step b), what was the DC offset of the waveform that you measured? How could you account for any value other than zero?
- 2) Regarding the AC measurement made in this section: Note in parts b and c, the values obtained from both the Agilent and Triplet meters were close to the source voltage; whereas in parts d and e, the Agilent value was accurate but the Triplet value was not. This result is due to the much larger input resistance of the Agilent meter. The first measurement made by the Triplet meter was (fairly) accurate because its input resistance is much larger than the 50Ω internal resistance of the function generator; but, the second Triplet measurement was not accurate because the meter does not have an input resistance much larger than the $10\text{ k}\Omega$ resistor. For this measurement, calculate what the Triplet meter should have read and compare it to what the meter actually did read. (For this purpose, you need to use the specified internal impedance of the Triplet meter. Note that the internal resistance of the Triplet is specified in Ω/volt , and hence varies depending on the scale you use—e.g., a 12-volt scale will have four times more internal resistance than the 3-volt scale.) How does this percent difference compare to the accuracy of the meter?

Note: You should have three different circuits [2), 3), and 4)] along with four sets of calculations [two for 2), and one each for 3) and 4)] for this section.

Section 3) Interference Signals and Shielding

Capacitive, inductive, radio frequency and ground loops interferences²

When taking measurements, in particular of low-level signals, you will notice that the signal often includes a lot of noise. This is usually due to interference from electric and magnetic sources which are present in the laboratory or in nearby spaces, and the fact that the noise amplitude is comparable to the small signal amplitude. This can include interference from fluorescent lights, switching power supplies, motors, a radio transmitter, or even faulty grounding (ground-loop interference). Here are a few precautions that can be taken to reduce the effects of interference.

- **Capacitive interference** is the result of wires at different voltages placed in close proximity to each other. When the voltage changes in one wire, a voltage can be induced in the neighboring one through capacitive coupling. Examples are wires coming from equipment such as function generators and oscillators, and wires from an outlet (60 Hz). The higher the frequency of the interfering source, the larger the interference will be. Another source of capacitive interference is fluorescent lamps. The best way to prevent capacitive interference is to use *shielded or coaxial cable*. The shield around the cable is usually connected to ground and protects the inner signal-carrying conductor from the interference.
- **Inductive interference** is the result of time varying currents in a conductor such as coils. It is not always easy to prevent this type of interference. If possible, one should work a distance away from such sources or shield the source with a ferromagnetic shield. Also, maintaining an appreciable distance between large current carrying wires and small-signal carrying wires, and positioning current carrying wires perpendicular to one another typically reduces inductive interference.
- **Radio frequency (RF) interference** is the result of radio transmitters and arcing in motors. To reduce the interference, one can shield the low-power signal carrying wire with a conducting shield connected to ground.

² Partially adopted and edited from “Signal Interference and Shielding.” Courtesy of University of Pennsylvania ESE department

- **Ground loop interference** is the result of voltage differences which often exists in the ground plane to which the circuits are connected. This can be eliminated by connecting all ground points in the circuit to a single earth ground.

Another good practice to reduce interference is to use short lengths for small signal lines and to keep their positions fixed. If necessary, bond the wires to the chassis (or to the lab bench for his experiment).

Experimental procedure

- Connect two test leads together at one end, and plug the other ends into the multimeter to form a complete loop.
- Move the loop around slowly, rotating its axis to find the maximum and minimum steady state voltages. Record these values. Note: keep your wire loop fully open (i.e., approximately circular) while changing its orientation. Turn on the oscilloscope and then drape the leads over and across this instrument; record the maximum value of the voltage induced in the leads.
- Twist the leads together over the entire length with about one crossover every three inches. Repeat the measurement in the part b.
- Leaving the test leads twisted, open the ends and connect them to the terminals of a decade box. Set the resistance successively to 0 Ω , 100 Ω , 1 k Ω , 10 k Ω and 100 k Ω . At each resistance setting, touch the decade box with your finger and record the steady state voltage observed. Note that you should press hard when making contact with your finger.

Section 4) Ground Loops

- Disconnect the multimeter leads from the decade resistance box and short them together (leads still twisted). Record the voltage displayed on the multimeter.
- Disconnect and untwist the leads, then connect the positive terminal of the multimeter to the ground terminal of the FG. Note that the negative terminal of the multimeter and the positive terminal of the FG are left open. Record the voltage. Turn off the FG; does this change the value of the voltage measured? If so, record it.

Questions: Section 4

- Any increase in voltage from step a) to step b) is caused by noise picked up in the ground loop. Draw a diagram of the effective circuit used in part b) which clearly shows the ground loop that exists. Explain how unwanted voltages are induced.