

DESIGN CONSIDERATIONS FOR ISOLATING AN I²C BUS OR SMBUS

1. Introduction

I²C (inter-integrated circuit bus) was developed in the early 1980s¹. In the early 1990s, Intel created an enhanced version of I²C called SMBus² (system management bus) for power and thermal management systems in server and PC applications. In the early 2000s, SMBus² was chosen as the physical interface for PMBus, an open specification for managing modular power systems, opening yet another market for I²C /SMBus products. Today, the venerable I²C bus continues to grow in popularity because of its low cost and overhead, strong industry support and relatively efficient communication protocol. As a result, I²C has been adopted in many new end applications.

In many of these applications, I²C/SMBus interfaces require galvanic isolation for safety or ground loop elimination. For example, Power over Ethernet (PoE) applications typically use an I²C interface for communication between the PoE power sourcing device (PSE) and the earth-ground-referenced system controller. Galvanic isolation is required both by standard and also as a practical matter to prevent ground loops in Ethernet connected equipment.

The physical interface consists of two wires: serial data (SDA) and serial clock (SCL). These wires are connected to open collector drivers that serve as both inputs and outputs. At first glance, it appears that SDA and SCL can be isolated simply by placing two unidirectional isolators in parallel and in opposite directions. However, this technique creates feedback that latches the bus line low when a logic low is asserted by either master or slave. This problem can be remedied by adding anti-latch circuits³ but results in a larger, more expensive solution.

Recent breakthroughs in silicon RF isolation technology enable both the isolation and anti-latch functions to be integrated in single packages, such as the Silicon Laboratories Si8400 and Si8405 I²C bidirectional isolators⁴. These products offer a single-chip, anti-latch solution to the problem of isolating I²C /SMBus applications and require no external components except the I²C /SMBus pull-up resistors. In addition, the devices provide isolation to a maximum of 2.5 kVACRMS, support clock stretching, and operate to a maximum bus speed of 2 Mbps.

This article describes the operation of integrated I²C isolators and the design constraints and considerations when using them.

2. I²C Isolator Operation

Without anti-latch protection, bidirectional I²C isolators latch when an isolator output logic low propagates back through an adjacent isolator channel creating a stable latched low condition on both sides. Anti-latch protection is typically added to one side of the isolator to avoid this condition (the "A" side for the Si8400/05). To prevent the latch condition, the "A side" output low (V_{OL}) and input low (V_{IL}) levels are designed such that the isolator V_{OL} is greater than the isolator V_{IL} .

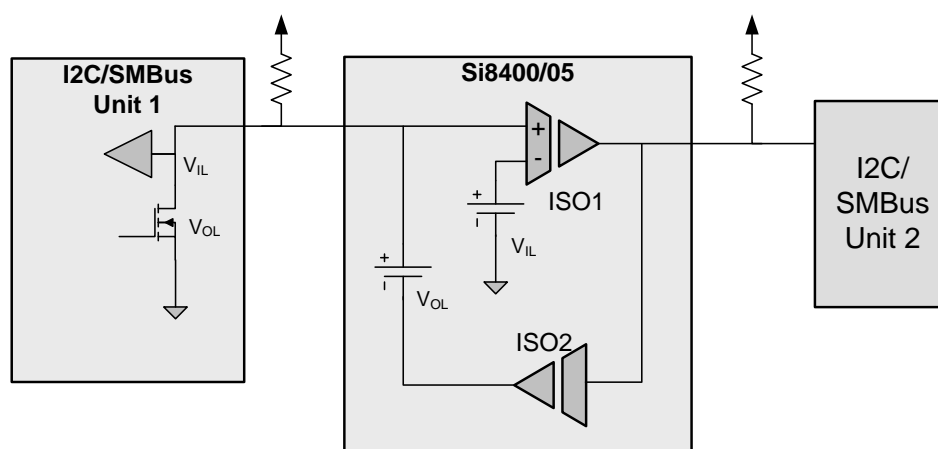


Figure 1. I²C Example Implementation Using the Si8400/05

2.1. I²C Isolator Design Constraints

Table 1 details the design constraints to consider when designing with I²C.

Table 1. I²C Design Constraints and Effects

Design Constraint	Data Sheet Values	Effect of Bus Pull-up Strength and Temperature
To prevent the latch condition, the isolator output low level must be greater than the isolator input low level.	Isolator V_{OL} 0.8 V typical Isolator V_{IL} 0.6 V typical Input/Output Logic Low Level Difference ΔV_{SDA1} , ΔV_{SCL1} = 50 mV minimum	This is normally guaranteed by the isolator data sheet. However, if the pull up strength is too weak, the output low voltage will fall, and it can get too close to the input low logic level. These track over temperature.
The bus output low must be less than the isolator input low logic level.	Bus V_{OL} = 0.4 V maximum Isolator V_{IL} = 0.45 V minimum	If the pull up strength is too large, the devices on the bus might not pull the voltage below the input low range. These have opposite temperature coefficients. Worst case is high temperature.
The isolator output low must be less than the bus input low.	Bus V_{IL} $0.3 \times V_{DD}$ = 1.0 V minimum for V_{DD} = 3.3 V Isolator V_{OL} = 0.825 V maximum, 0.5 mA pullup -10°C to 125°C	If the pull up strength is too large, the isolator might not pull the below-the-bus input low voltage. Si8400/05 Vol: -1.8 mV/C CMOS buffer: -0.6 mV/C This gives some temperature tracking, but worst case is cold temperature.

2.2. I²C Isolator Design Considerations

The first step in applying an I²C isolator is to choose which side of the bus will be connected to the isolator A side. Ideally, it should be the side that:

1. Is compatible with the range of bus pull up specified by the manufacturer. For example, the Si8400/05 isolators are normally used with a pull up of 0.5 to 3 mA.
2. Has the largest input low level for devices on the bus. Some devices may specify an input low of 0.9 V, and other devices may require an input low of $0.3 \times V_{DD}$. Assuming a 3.3 V minimum power supply, the side with an input low of $0.3 \times V_{DD}$ is the better side because this side has an input low level of 1.0 V.
3. Has devices on the bus that can pull down below the isolator input low level. For example, the Si840x input level is 0.45 V. Since most CMOS devices can pull to within 0.4 V of GND, this is generally not a problem.
4. Has the lowest noise. Due to the special levels, noise margins are reduced to as low as 50 mV.

The Si840x isolators are not compatible with devices that have a logic low of 0.8 V. For this situation, a discrete circuit can be used.⁵

2.3. Other System Level Design Considerations

Two other important system level design considerations are clock stretching and accommodation of additional system status and control signals that typically require isolation.

It is clear that the data line (SDA) needs to be bidirectional as this line contains data that can be either from the host to the slave or from the slave to the host. It is also common practice for the slave device to hold the clock line (SCL) low during the "acknowledge" (ACK) period while it is retrieving data for the master. For "clock stretching" to work in a particular I²C design, an I²C isolator that is also a bidirectional channel on the SCL line must be used. Without bidirectional isolation on the SCL signal, the designer must ensure that all I²C slaves can operate with the same bus clock rate and timing characteristics as the master. This places additional design and validation burdens on the system developer. The Si8400 is bidirectional for both SCL and SDA.

Besides SCL and SDA signal isolation, many designs also require additional system status and control signals, such as resets and interrupt lines, to be isolated. The use of monolithic I²C isolators with additional unidirectional channels allows the system designer to simplify timing challenges in a design. Instead of being forced to isolate additional status and control channels in multiple isolator or opto-coupler packages (which results in significant part-to-part timing variations), monolithic I²C isolators with extra unidirectional channels exhibit timing characteristics that track very closely across process, voltage and temperature variations. The Si8405 has two additional unidirectional channels that are useful for isolating reset and interrupt signals.

I²C design does not have to be a mystery. By considering each of these design tips and choosing an isolator appropriate to the demands, designers can easily implement I²C in their products.

3. References

1. NXP UM102104, I²C-bus specification and user manual, Rev. 03 - 19 June 2007
2. SMBus.org, "System Management Bus (SMBus) Specification", Version 2.0, August 3, 2000
3. John Gammel, "Adding bidirectional I²C digital isolation to your embedded design" Embedded.com Jan 30, 2009
4. Silicon Laboratories, Inc., Si8400/05 data sheet.
5. Silicon Laboratories, Inc., "AN352: Low-Cost, High-Speed I²C Isolation with Digital Isolators".

DOCUMENT CHANGE LIST

Revision 0.1 to Revision 0.2

- Updated V_{IL} and V_{OL} levels to be consistent with latest data sheet.

NOTES:

CONTACT INFORMATION

Silicon Laboratories Inc.

400 West Cesar Chavez

Austin, TX 78701

Tel: 1+(512) 416-8500

Fax: 1+(512) 416-9669

Toll Free: 1+(877) 444-3032

Email: productinfo@silabs.com

Internet: www.silabs.com

The information in this document is believed to be accurate in all respects at the time of publication but is subject to change without notice. Silicon Laboratories assumes no responsibility for errors and omissions, and disclaims responsibility for any consequences resulting from the use of information included herein. Additionally, Silicon Laboratories assumes no responsibility for the functioning of undescribed features or parameters. Silicon Laboratories reserves the right to make changes without further notice. Silicon Laboratories makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Silicon Laboratories assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. Silicon Laboratories products are not designed, intended, or authorized for use in applications intended to support or sustain life, or for any other application in which the failure of the Silicon Laboratories product could create a situation where personal injury or death may occur. Should Buyer purchase or use Silicon Laboratories products for any such unintended or unauthorized application, Buyer shall indemnify and hold Silicon Laboratories harmless against all claims and damages.

Silicon Laboratories and Silicon Labs are trademarks of Silicon Laboratories Inc.

Other products or brandnames mentioned herein are trademarks or registered trademarks of their respective holders.