

AN49947

Associated Part Family: CY14BXXXX/STK17TX8
[GET FREE SAMPLES HERE](#)

Application Note Abstract

This application note describes the undershoot effect in the RTC circuit of the 256K and 1M nvSRAM in 0.25μ technology. The part numbers affected are CY14B256K/STK17T88 and CY14B101K/STK17TA8.

Introduction


Under certain noise conditions, the Real Time Clock (RTC) circuit of CY14BXXXX/STK17TX8 can be disturbed to the point that the oscillator circuit stops.

Undershoot in Application

The RTC devices in 0.25μ specify in the data sheet that inputs may not undershoot by more than -0.5V. This is difficult to achieve in systems where signal fall times are fast (1 to 3 ns). As a result of these fast fall times, signal undershoot greater than -0.5V is quite common.

Signal undershoot greater than -0.5V causes the ESD diodes on the device inputs to conduct current. This current travels through the substrate until it reaches collection points (guard bands with substrate contacts). However, as this current flows within the substrate, it adds noise to the overall noise floor on the device.

Figure 1. Signal Undershoot

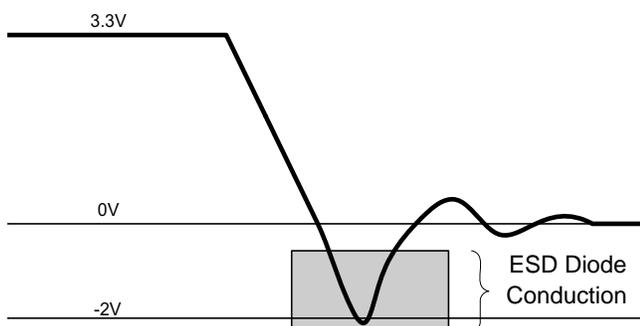

Effect on RTC Oscillator

The RTC oscillator circuit, which is embedded on the 256K and 1M nvSRAM family is designed to be a very low power circuit. To achieve this low power operation, the automatic gain circuit of the oscillator is designed to operate on very small currents (nano-Amperes). This makes the gain circuit sensitive to on-chip noise, which in turn makes the RTC oscillator circuit very sensitive to substrate currents caused by signal undershoot.

There have been reports of the oscillator stopping in some customer systems. Investigation showed that these systems all had a significant amount of undershoot. Correcting the undershoot on the input pins corrected the problem. The address pins A₀-A₃ and data pin DQ₀ are located in the area of the RTC oscillator circuit. Undershoot on these address pins has the greatest effect on the RTC circuit operation. It is recommended that customers experiencing similar problems investigate and correct undershoot issues.

Recommendation

Undershoot can be reduced by adding a Schottky diode ($V_F < 0.4V$ with I_F at 100 mA) connected with the anode at ground and cathode on the signal line as close to the device pin as possible. Layout must route the signals to connect to the diode first then the pin if possible. The anode to ground should go directly to the ground plane. The only signals that require this treatment are A₀, A₁, A₂, A₃, and DQ₀. A scope must be used to confirm controlled undershoot as some fast edge rates may need more effective termination. It is critical that the voltage does not go below 0.6V as substrate currents begin to flow.

Document History

Document Title: Undershoot Effect in RTC Circuit of 0.25 μ nvSRAM

Document Number: 001-49947

Revision	ECN No.	Orig. of Change	Submission Date	Description of Change
**	2606848	NXR	11/13/08	New application note

All trademarks or registered trademarks referenced herein are the property of their respective owners.

Cypress Semiconductor
 198 Champion Court
 San Jose, CA 95134-1709
 Phone: 408-943-2600
 Fax: 408-943-4730
<http://www.cypress.com>

© Cypress Semiconductor Corporation, 2008. The information contained herein is subject to change without notice. Cypress Semiconductor Corporation assumes no responsibility for the use of any circuitry other than circuitry embodied in a Cypress product. Nor does it convey or imply any license under patent or other rights. Cypress products are not warranted nor intended to be used for medical, life support, life saving, critical control or safety applications, unless pursuant to an express written agreement with Cypress. Furthermore, Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress products in life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

This Source Code (software and/or firmware) is owned by Cypress Semiconductor Corporation (Cypress) and is protected by and subject to worldwide patent protection (United States and foreign), United States copyright laws and international treaty provisions. Cypress hereby grants to licensee a personal, non-exclusive, non-transferable license to copy, use, modify, create derivative works of, and compile the Cypress Source Code and derivative works for the sole purpose of creating custom software and or firmware in support of licensee product to be used only in conjunction with a Cypress integrated circuit as specified in the applicable agreement. Any reproduction, modification, translation, compilation, or representation of this Source Code except as specified above is prohibited without the express written permission of Cypress.

Disclaimer: CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS MATERIAL, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. Cypress reserves the right to make changes without further notice to the materials described herein. Cypress does not assume any liability arising out of the application or use of any product or circuit described herein. Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress' product in a life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

Use may be limited by and subject to the applicable Cypress software license agreement.