

ISSUE: August 2012

Testing Power Supply Compliance To Energy Efficiency Standards

by Silvestro Fimiani, Power Integrations, San Jose, Calif.

Over the last several years, leading worldwide standards organizations, including the Environmental Protection Agency's Energy Star program, the European Commission's Code of Conduct and the California Energy Commission (CEC), have defined new efficiency requirements for external power supplies. These standards demand that designers test their products for active-mode efficiency and no-load power consumption to high levels of accuracy. To help simplify that process and accelerate product development, this article will describe a relatively straightforward way to measure compliance to these evolving energy efficiency standards and offer a few testing tips.

Basic Requirements

We'll begin with the equipment needed to perform these tests. You will need four components to accurately measure your product's efficiency:

- 1. A wattmeter
- 2. A programmable ac source
- 3. An electronic load
- 4. Two digital multimeters (one must be a high-resolution current meter)

Next, a few general guidelines will help you achieve accurate results. First, since the energy efficiency compliance measurement of a power supply is a system-level test that includes losses in the input and output cables, you must ensure that the same cables used in this testing process are used in the final product. Second, it is important to note that these tests require long temperature-stabilization periods between output line and input line voltage changes. Therefore, expect the tests to take several hours to complete. Finally, every time you alter your product design, these tests must be repeated to ensure accurate results.

Maximizing Accuracy

This test requires measurement of both no-load input power and active-mode efficiency of the supply. To calculate efficiency one must measure both input and output power. When measuring input power, the selection of the proper power source is crucial. As the graph in Fig. 1 illustrates the use of raw ac power from a wall outlet and Variac introduces inaccuracy into the measurement. To ensure the testing is performed at a precise input voltage, use a programmable ac source instead.

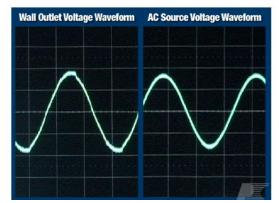


Fig. 1. Comparison of raw mains ac quality vs. a programmable ac power source.



The graph in Fig. 2 depicts the output from a programmable ac source. Note the incoming waveform is a pure sine wave.

 $\mathbf{P} = \mathbf{V} \times \mathbf{I} \times \mathbf{COS} \boldsymbol{\varphi}$

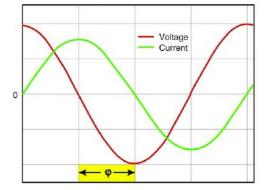


Fig. 2. Power factor = cosine of phase angle between voltage and current waveform.

To make this measurement we use a wattmeter because it factors in the effect of power factor, cosine of the angle between the voltage and current waveforms ($\cos \phi$). It is important to note that the energy efficiency standard demands an input-power-measurement uncertainty of less than 2% for power measurements of 0.5 W or greater and 10 mW for power measurements less than 0.5 W.

Wattmeters from several leading instrument manufacturers can be configured to meet these requirements. Since a wattmeter features both a current- and voltage-sensing element, the voltage-sensing element can be configured either before or after the input current-sense element. Typically, information on how to configure the instrument can be found in its user manual. For low- or no-load measurements, you can achieve better accuracy by configuring the voltage sense before the current-sense element. This prevents the current from the voltage-sense element from being measured by the current-sense element. Given that the current consumed by the voltage-sense element is typically greater than the allowable 10 mW at 230 Vac, this configuration is critical to meeting the standard's low measurement-uncertainty requirements.

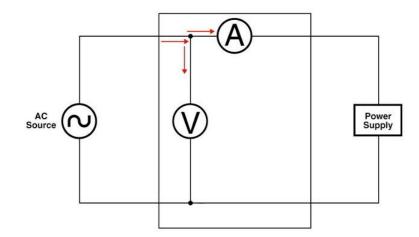


Fig. 3. Wattmeter connections. Connect voltage sense before current sense for low or no-load measurements.

High-Power Applications

Higher-power designs present different issues. In these applications the power loss in the voltage-sense element is so small, the voltage-sense element can be connected after the current sense to locate it close to the power supply input. This approach prevents the voltage drop across the current-sense element and the internal © 2012 How2Power. All rights reserved. Page 2 of 6



wiring of the wattmeter from being incorrectly included in the power measurement. That, in turn, can lead to lower efficiency calculations. By setting the meter to average over 32 (or 64) samples you can generate more stable results.

You will need two multimeters to measure output power; one to measure output voltage and the other to measure current. Use the higher-resolution meter to measure current. Since output power is purely dc, it is calculated by multiplying output voltage times output current.

To simplify the task of determining whether the specifications of your power supply comply with worldwide regulations, Power Integrations has developed a helpful <u>Energy Compliance Calculator</u>. The targets for no-load and active-mode efficiency are derived from the nameplate rating of each power supply. That rating is simply the rated output marked on the power supply case and represents the minimum rated output power of the supply at room temperature and nominal line. As an example: a constant-voltage, constant-current charger with a nameplate rating of 5 V, 350 mA will deliver 5 V, 350 mA minimum.

Once you enter the nameplate output power rating for your power supply, the calculator will automatically tell you the target values for compliance to the energy standards relevant to your design. Designs that accept universal input voltages require measurements made at both 115 Vac, 60 Hz and 230 Vac, 50 Hz. Measurements for single-input designs should be made at the nominal line voltage of either 115 Vac or 230 Vac.

To demonstrate this process let's look at the test procedure for a 5-V, 350-mA cell phone charger rated for universal input. We begin with a series of tests to measure active-mode efficiency at 115 Vac, 60 Hz. Active-mode efficiency is the average of efficiencies measured at 25%, 50%, 75% and 100% of the nameplate rating at a nominal line-input voltage and nominal line frequency. Since the nameplate load rating of this charger is 350 mA, efficiency must be measured at the following currents: full load (350 mA), 75% load (262 mA), 50% load (175 mA) and 25% load (88 mA.)

Begin the test process by warming up the power supply for 30 minutes. To make the first measurement at 100% load, connect the power supply to an ac source and apply a 60-Hz, 115-Vac input. Gradually increase the load on the power supply to 100% and allow at least 30 minutes for the circuit to reach thermal equilibrium and the input power reading to stabilize. Before recording any measurements, make sure no oscilloscope probe or other meter is connected to the circuit. In some cases you may need to manually set the voltage and/or current range of the wattmeter to prevent it from auto-ranging and giving fluctuating results. The same measuring instrument, in two different ranges, will typically have different levels of accuracy. Typically, the operator's manual will indicate the range that will generate the highest accuracy.

Once the circuit has reached thermal equilibrium, take the initial power reading from the wattmeter. Wait five minutes and then take a second reading. If you find less than 5% difference between the two readings, record the second reading. If the difference is larger than 5%, you should wait another five minutes and continue to do so until two successive readings are within 5% of one another. Alternatively, you can use the "integration mode," available on most wattmeters and described in the following section.

Calculating Integral Input Power

To measure the input power of a design where the input power varies over time, take the following steps:

- 1. Set your wattmeter to integration mode.
- 2. Set the interval of integration for your wattmeter to capture approximately one full cycle of variable input power. (The longer the duration, the higher the accuracy of results. We recommend integrating over a period of 1 minute for most applications.)
- 3. Read the input energy from your wattmeter as W-hr.
- 4. Divide this number by the interval of integration. Make sure to adjust the time units so they cancel. For example:

Input Energy (W-hr)/Measurement Interval (min) * 60 mins/1 hr = Input Power (W). © 2012 How2Power. All rights reserved.



In this example, the output current is recorded as 0.35 A and the output voltage is 6.124 V from the multimeters, giving an output power of 2.14 W.

Efficiency is calculated as:

Efficiency at full load = Pout/Pin
=
$$2.14 \text{ W}/3.14 \text{ W}$$

= 68.2%

To make the next measurement, adjust the load to 75% or 262 mA. When using the averaging feature on the wattmeter, remember to allow at least one minute for the reading to stabilize. Then, record the input power from the wattmeter. Wait five minutes, record again and use the <5% difference rule to decide whether to use the value or calculate the integral input power.

In this example, the output current is recorded as 0.262 A and the output voltage is 6.502 V, giving an output power of 1.704 W. Efficiency is then calculated as:

Efficiency at 75% load =
$$1.704 \text{ W}/2.42 \text{ W}$$

= 70.4%

This procedure should then be repeated for 50% and 25% load levels.

Measuring No-Load Input Power

To measure no-load input power, disconnect the output load and all output multimeters from your power supply. Next, turn off the ac input and configure your wattmeter with the voltage-sense element before the current-sense element. Take an initial power reading from the wattmeter and wait five minutes before taking a second reading. As we have discussed in previous test procedures, record the second reading if the difference between the two readings is less than 5%. If not, you must integrate the input power and divide by the time period of integration using the process we described earlier.

This completes testing at 115 Vac. Next, you must reattach your load and output multimeters and increase the input voltage to 230 Vac. Repeat all the previous tests at the new line voltage. Remember to set up your wattmeter appropriately for your power range. Once testing is complete you should have a complete set of data listing the results for all four load levels at both line voltages. (To ensure accurate measurements when changing line voltage, see the tip "Changing Input Voltage" in the appendix.)

At this point you can open the Efficiency Compliance Calculator and enter the nameplate specification in the top input fields and the newly generated test data in the columns on the left side (Fig. 4.)



Enter Power Supply Specification: Output Voltage (V) Output Current (A) Input Voltage (VAC)				External Power Supply Efficiency Compliance Calculator by			
5	0.35	Universal			INTEG	RATIONS	
Nameplate Power (W)	: 1.75	Enter the specifications, n mode efficiency data for y current worldwide energy	our pos	ver supply	to see if i		
115(VAC)	230(VAC)		No l	.oad	Active	1	
lo-load Input (W) 0.096	0.127		Req.	Actual	Req.	Actual	
	-	ENERGY STAR (v2)	0.3	0.127	0.66	0.671	
Enter Input Efficiency:		EISA 2007			lo cc		
115(VAC)	230(VAC)	EISA 2007	0.5	0.127	0.55	0.671	
at 25%* 0.705 🚔	0.636	EC Code of Conduct (v4)*	0.3	0.127	0.66	0.671	
at 50%* 0.717	0.675	EC Ecodesign (EuP Tier 1)	0.5	0.127	0.55	0.671	
at 75%* 0.704	0.688	EC Ecodesign (EuP Tier 2)	0.3	0.127	0.66	0.671	
at 100%* 0.683	0.687	China USB Charger Spec (YD/T 1591-2006)	0.3	0.127	0.5	0.671	
Avg. Efficiency 0.7023	0.6715	*For mobile phone chargers <	8 W. no-k	ad power s (25		
* Enter percentage as a decimal.		EC Integrated Product Policy (IPP)		**	Four Stars (0.03 to 0.15 W)		
		s of <250 W only. While every effort To obtain most recent data, please		ublished stan	dards of spec		

Fig. 4. Data entered into PI Efficiency Compliance Calculator.

Power Integration's calculator computes active-mode efficiency as the equally-weighted average of efficiency across all load levels. The fields on the right side of the screenshot above show various efficiency standards. The calculator automatically calculates compliance requirements for active-mode efficiency and no-load input power and compares your test results with the standards requirements. To simplify analysis of results, it highlights those results that meet requirements in green and those that do not in red. (For those not using Power Integration's calculator to perform efficiency calculations, see the test tip "Calculating By Hand," in the appendix.)

Conclusion

As leading standards organizations focus on eliminating wasted power, they are developing increasingly stringent efficiency requirements for external power supplies. At the same time, efforts to synchronize these standards around the globe promise to bring conformity from region to region. By following the test methods outlined above, designers can ensure their power supplies meet these emerging regulations and take the first step to accessing worldwide markets.

Appendix

Test Tip: Calculating by Hand

If you decide to calculate values by hand, it is important to note that standards requirements are rounded to two digits for both no-load requirements and active-mode efficiency. This seemingly minor point can play a major role in standards compliance. Take the sample calculation below for minimum efficiency using the Energy Star formula for a 12-V, 1.1-A supply:

Nameplate power = $12 V \times 1.1 A = 13.2 W$

 $\eta_{\min} \ge [0.0626 \text{ x ln x (13.2)}]$

≥ 0.784 or 78.4%

 \geq 0.78 or 78% rounded to two digits

Now let's look at an example that shows the effect of rounding using measured results for the same 12-V, 1.1-A supply:



 $\eta_{avg} = (\eta_{25} + \eta_{50} + \eta_{75} + \eta_{100})/4$ = (79.2 + 78.4 + 75.9 + 80.5)/4 = 0.785 or 78.5% = 0.79 or 79% rounded to two digits

As the measured average is 79%, the power supply meets the standard's requirement of 78% efficiency.

Test Tip: Changing Input Voltage

Are you measuring no-load power consumption and planning to change input voltage during testing? Always apply full load to the output during this transition. Why? Under no load the input bulk capacitor takes a long time to discharge. If the output is left with no load connected when the input voltage is dropped from high line to low line, the capacitor will support the dc bus for a long period of time before drawing power from the ac input. That, in turn, causes the power supply to have a no-load input power of 0 W. To avoid this problem begin with the power supply fully loaded and only then remove all output loads before beginning the measurement.

About The Author



Silvestro Fimiani is product marketing manager of appliance and industrial applications at Power Integrations (PI). Prior to joining PI in 2005, Silvestro served as director of engineering of high-power products at International Rectifier. He holds a Bachelor of Arts in Physics from the University of Naples, Italy.

For further reading on power supply efficiency issues, see the <u>How2Power Design Guide</u>, select the Advanced Search option, go to Search by Design Guide Category, and select "Efficiency" in the Design Area category.